

# The Arithmetic-Logic Unit (ALU)

---

---

Combinational circuit that performs operations in CPU

Given inputs  $a$  and  $b$ , and an operation code, produce an output

Operation codes:

000: AND

001: OR

010: NOR

100: ADD

101: SUB

• • •

Unlike the adder, this is a general-purpose unit




# Subtraction

To calculate  $a - b$ , use  $a + (-b)$ .

To calculate  $-b$ , flip all the bits and add 1.

⇒ build it using an adder

 

Of course, *any* adder will do ...

– use block carry-lookahead adder from last time!




# Combined Add/Subtract Unit


Given: one bit of control  $c$ , two  $N$  bit inputs  $a$  and  $b$ .  
compute  $a + b$  if  $c = 0$ ,  $a - b$  if  $c = 1$ .

- Carry-in to the adder is  $c$
- one input:  $a$
- other input:  $b$  if  $c = 0$ , complement of  $b$  if  $c = 1$ .

Standard element: MUX (multiplexor)

 

# Combined Add/Subtract Unit

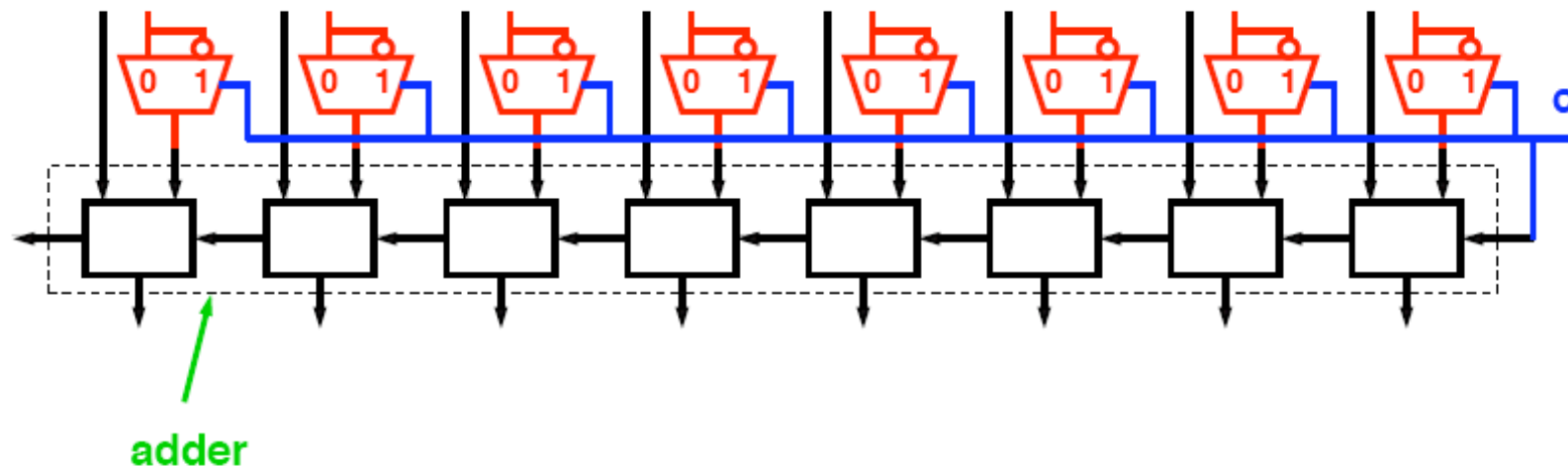

- Hierarchical design
- Reuse components
- Replication




# Shifter

---

4-input MUX?

Simple shifter:

 

# Arithmetic Logic Unit (ALU)

---

Example ALU: given inputs  $a$  and  $b$ , and an operation code, produce output.

Operation code:

- 000: AND
- 001: OR
- 010: NOR
- 011: ADD
- 111: SUB

How do we implement this ALU?




# Selecting An Operation

---


2-bit decoder: 2 bit input, 4 bit output

 - input: 00, output: 0001
- input: 01, output: 0010
- input: 10, output: 0100
- input: 11, output: 1000


 
# ALU: One Bit


Use decoder to select operation, and use combined add/subtract unit.




 
# ALU: Multiple Bits

Chain ALU *bit slices* to get an  $N$  bit ALU:



How can we use a better adder in the ALU?



# Overflow Detection

---

Overflow = result of operation cannot be represented

## Unsigned $N$ -bit addition:

- Overflow = result requires more than  $N$  bits  
⇒ carry-out of MSB is 1

## Signed addition:

- Adding two positive numbers
- Adding two negative numbers

Overflow  $\equiv$  carry-in to MSB  $\neq$  carry-out of MSB



# Comparison

---

## When is $a < b$ ?

- $a < b \equiv a - b < 0$
- Subtract  $b$  from  $a$ , check sign of result
- Sign bit is MSB


## When is $a = b$ ?

- $a = b \equiv a - b = 0$
- Subtract  $b$  from  $a$ , check if all bits are zero
- Use NOR gate





# Integer Multiplication: First Try

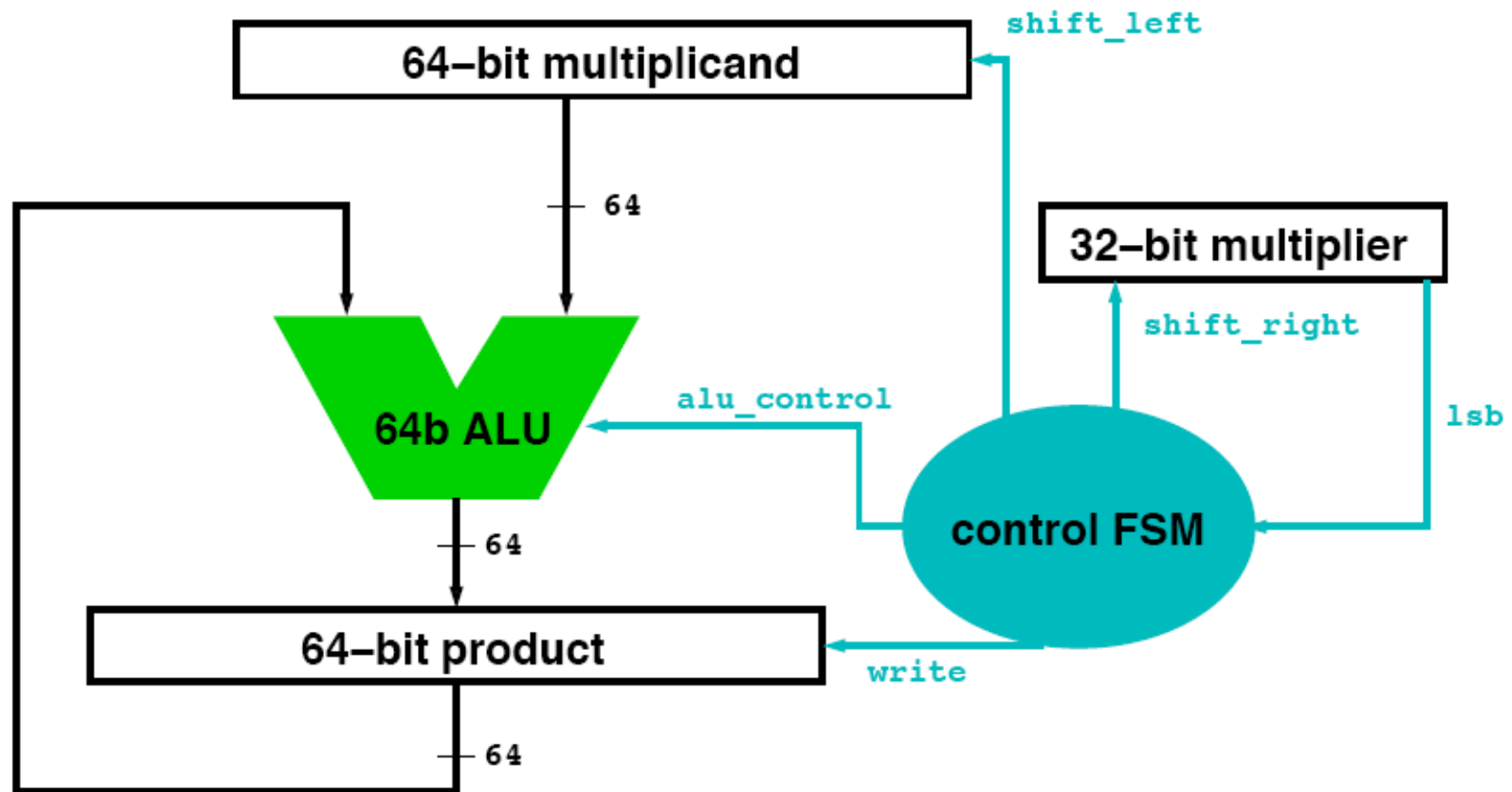


How do we build this?




# Registers And Shift Registers


Register with shift left:

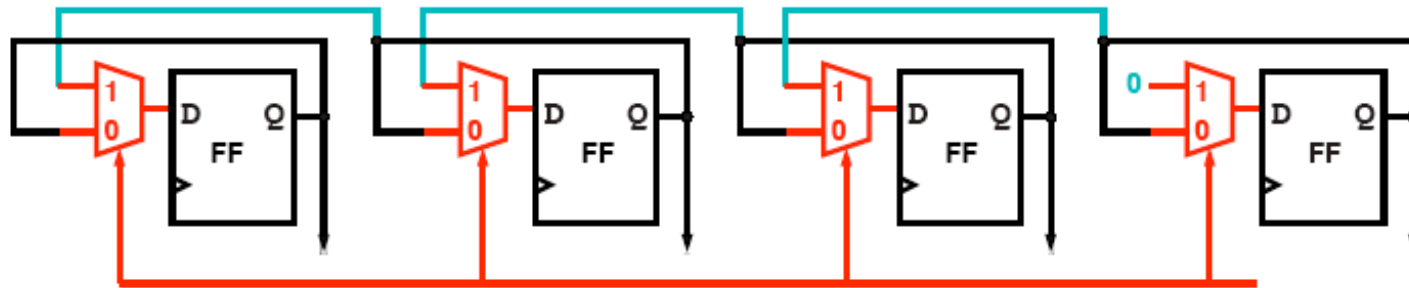

Register with write:

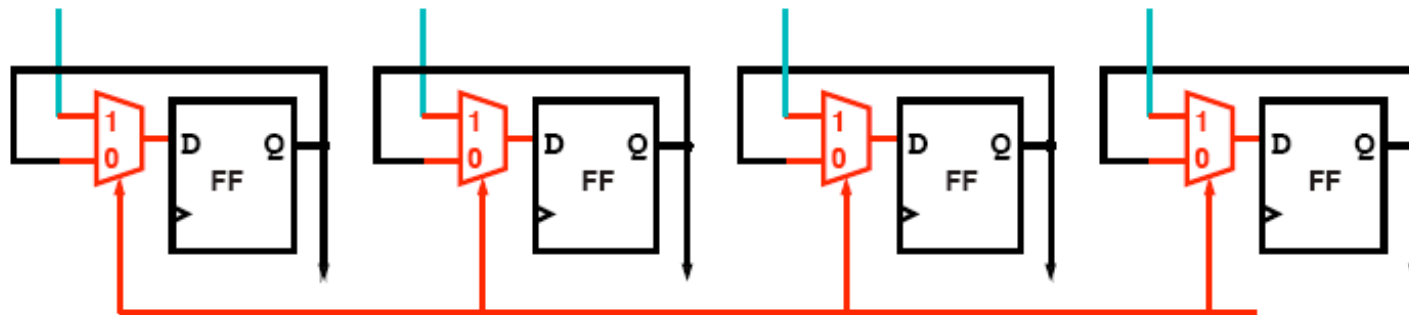

# Control

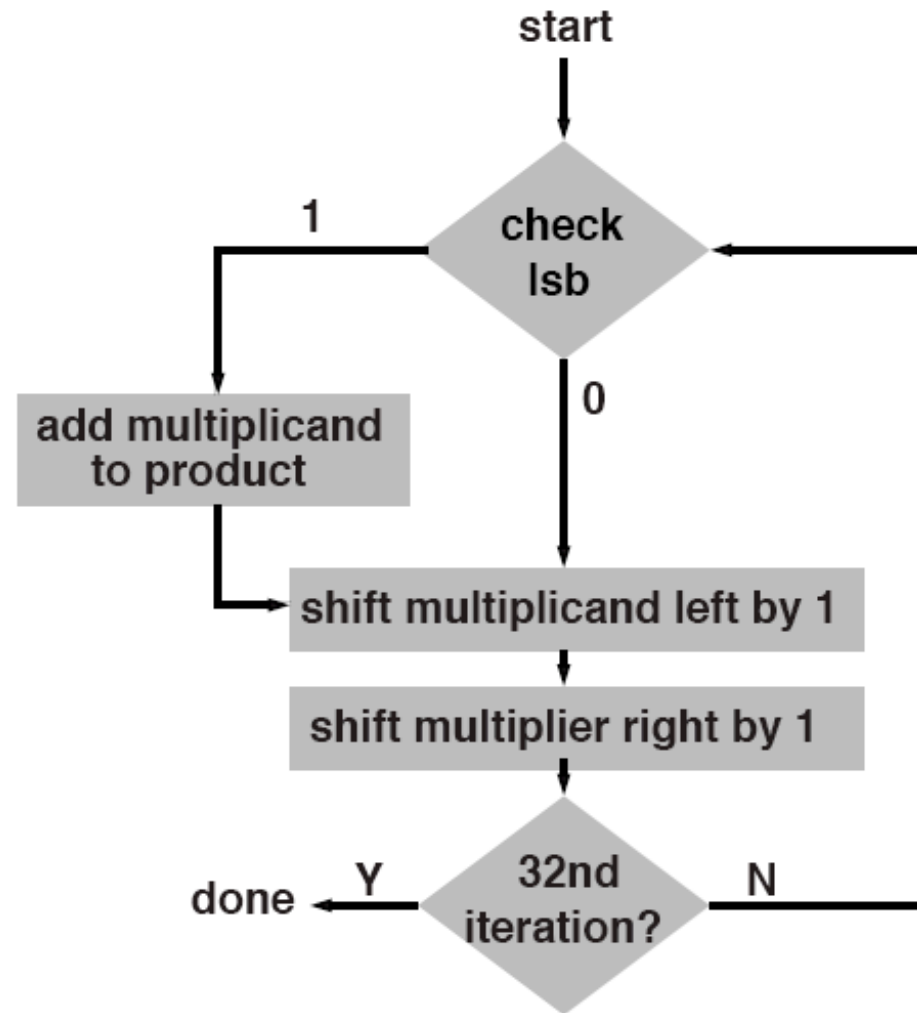

# Integer Multiplication

---


## Observations:

- 32 iterations for multiplication  $\Rightarrow$  32 cycles
- How long does 1 iteration take?
- Suppose 5% of ALU operations are multiply ops, and other ALU operations take 1 cycle.  
 $\Rightarrow CPI_{alu} = 0.05 \times 32 + 0.95 \times 1 = 2.55!$
- Half of the bits of the multiplicand are zero  
 $\Rightarrow$  64-bit adder is wasted
- 0's inserted when multiplicand shifted left  
 $\Rightarrow$  product LSBs don't change






# Using A 32-Bit ALU

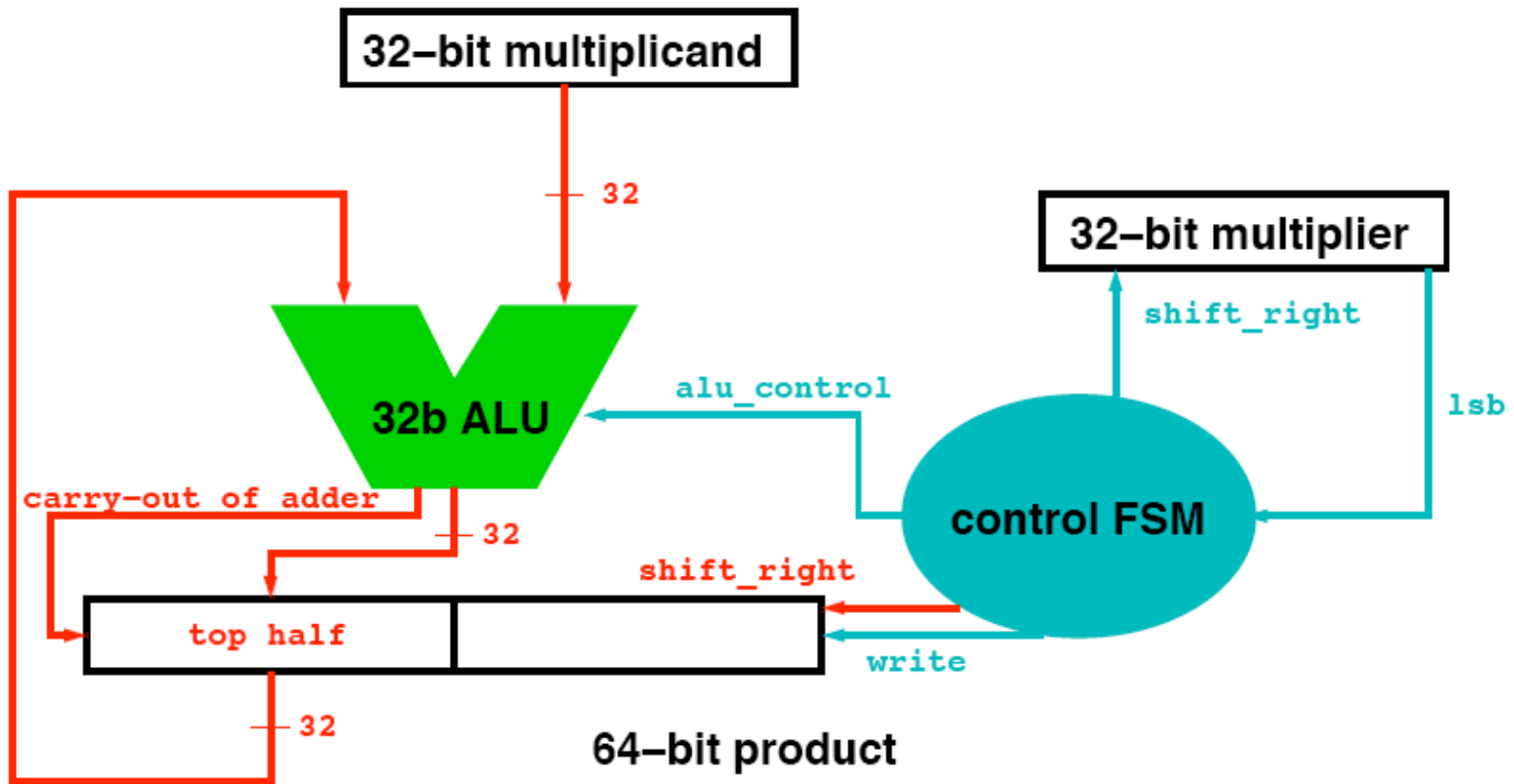

# New Control

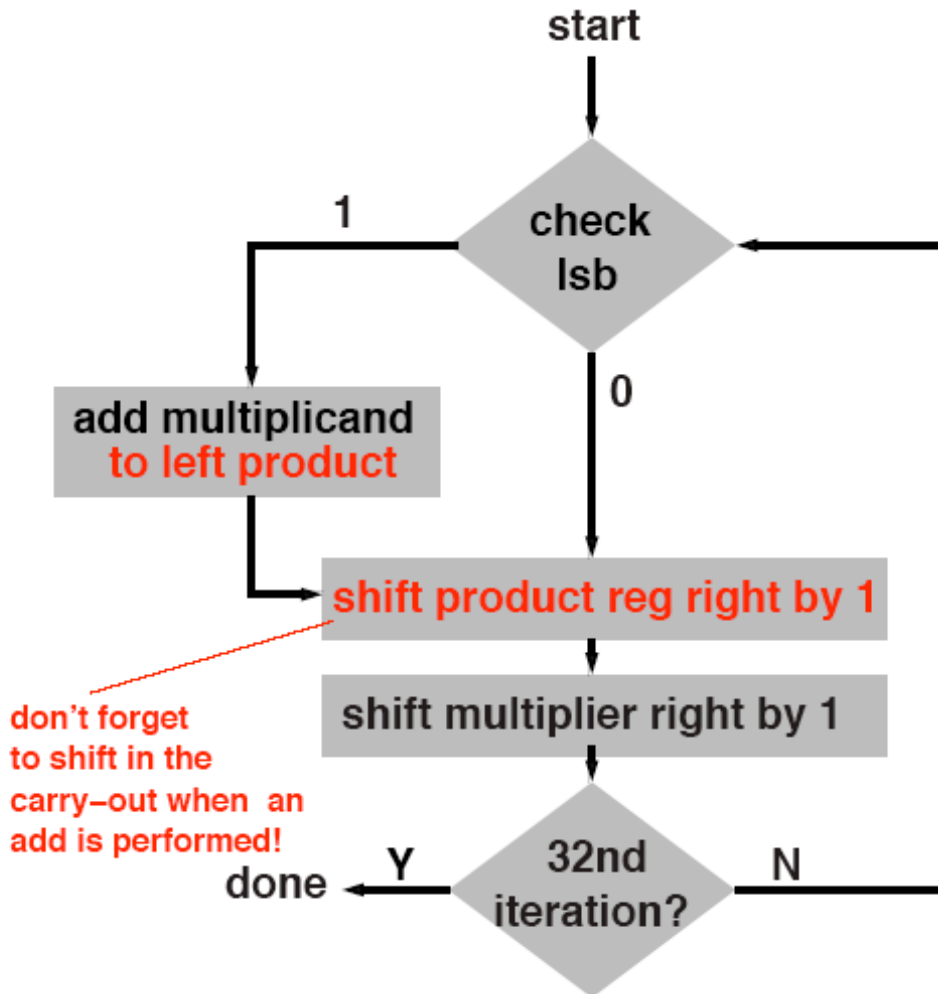

don't forget to shift in the carry-out when an add is performed!


Bottom half of product register is zero initially.

Each iteration:  
adds 1 product bit  
loses one multiplier bit


Share storage for product register and multiplier!




# Integer Multiplication Hardware

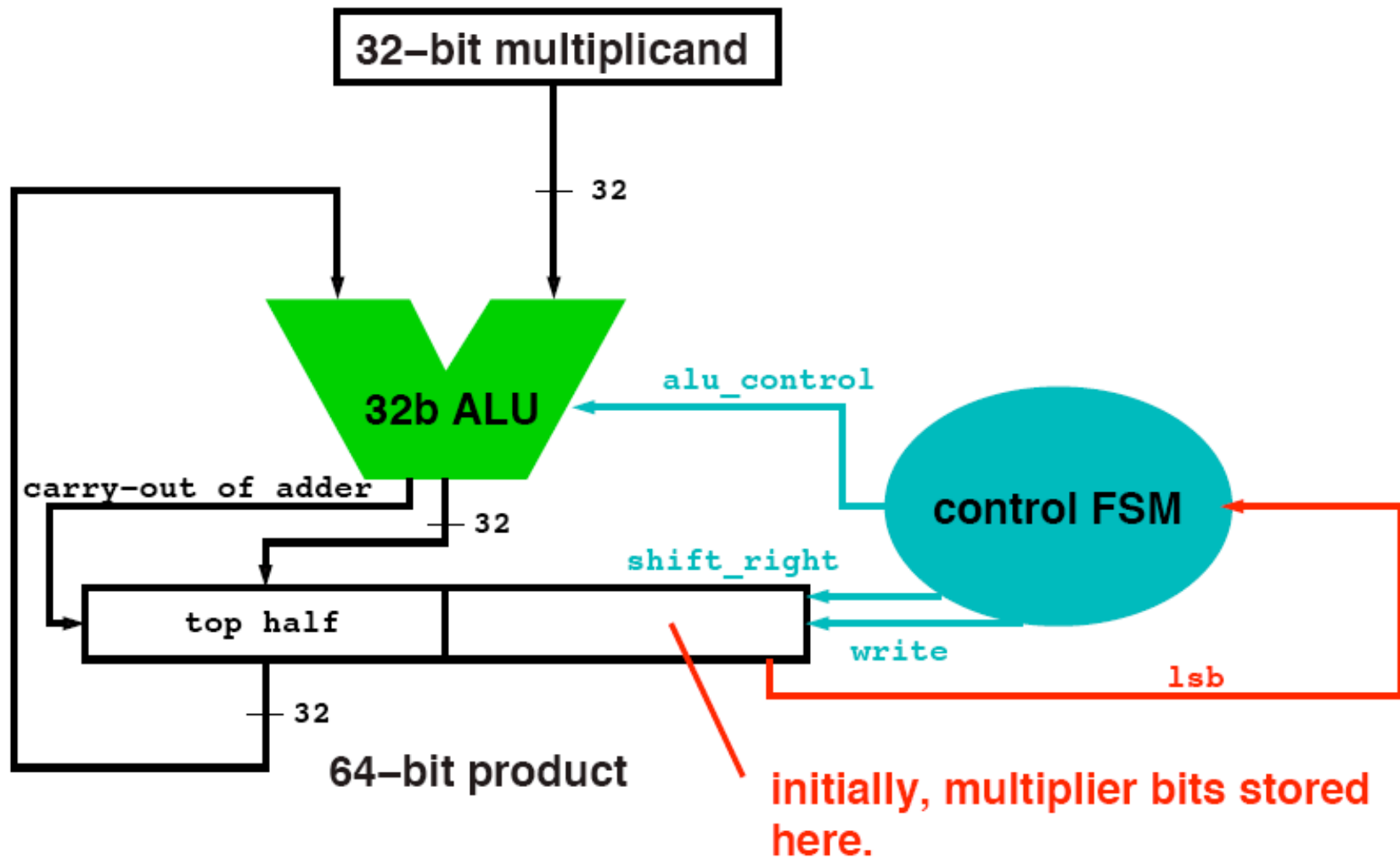


# Integer Multiplication Hardware

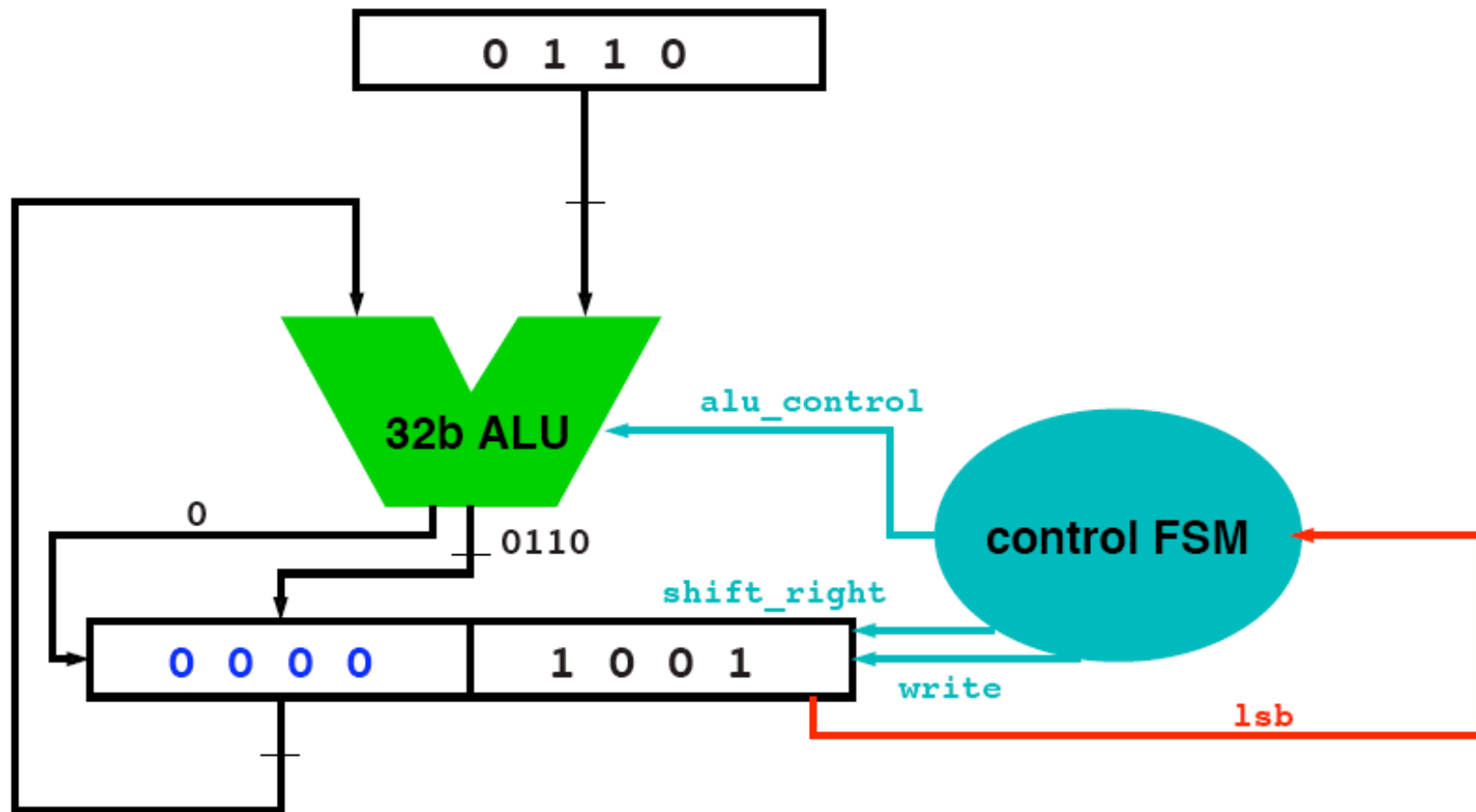


# Integer Multiplication Hardware

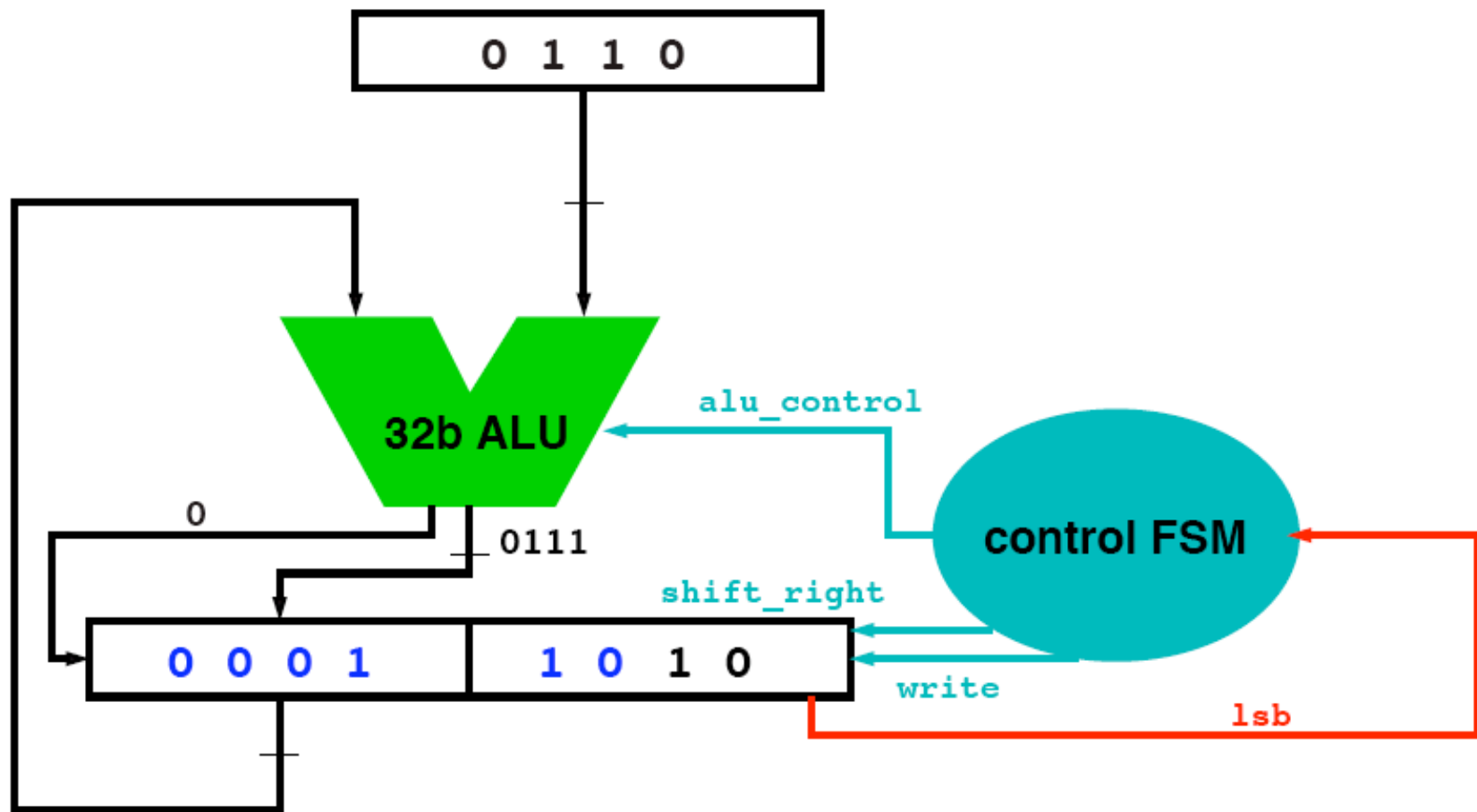

# Integer Multiplication Hardware

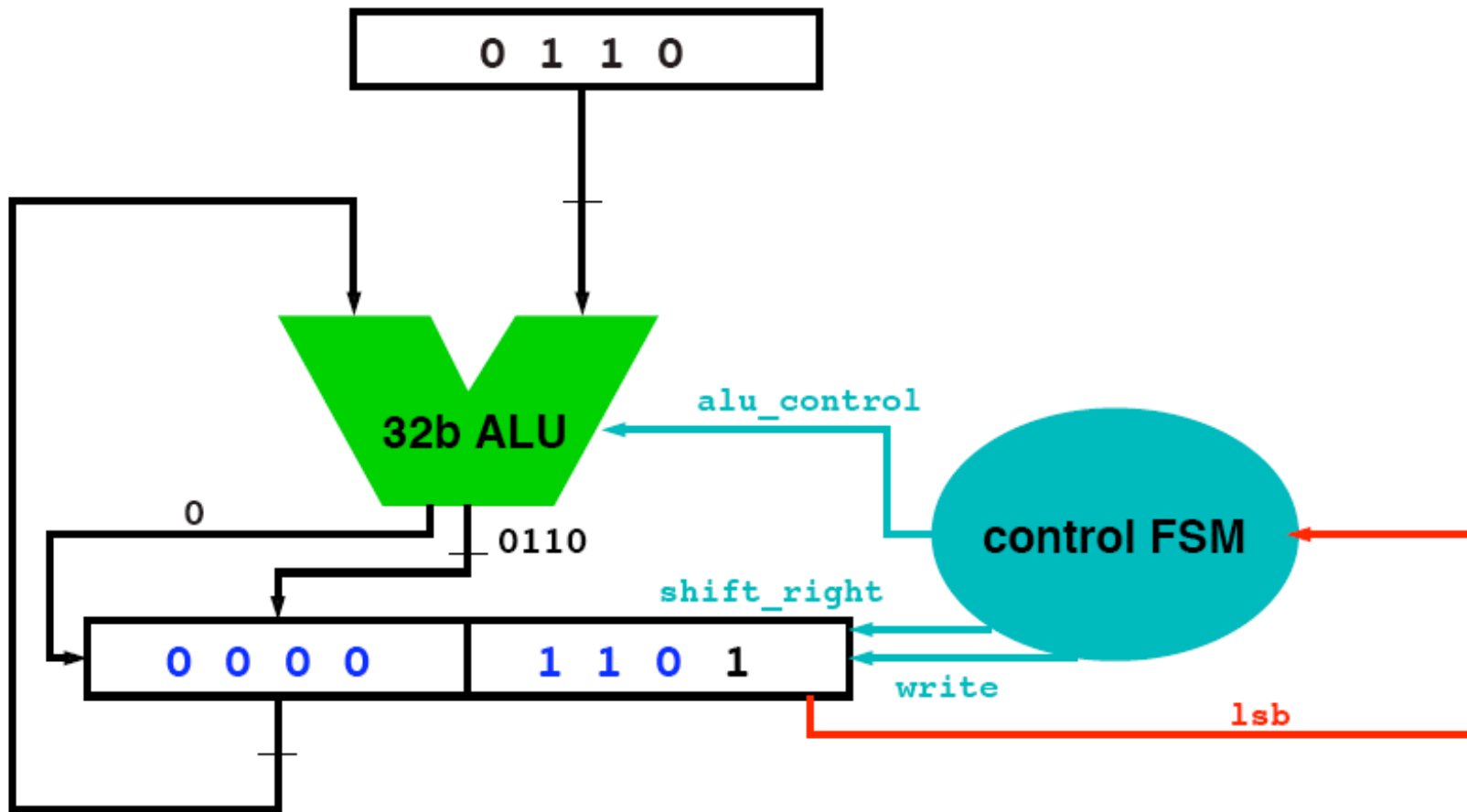

# Integer Multiplication Hardware

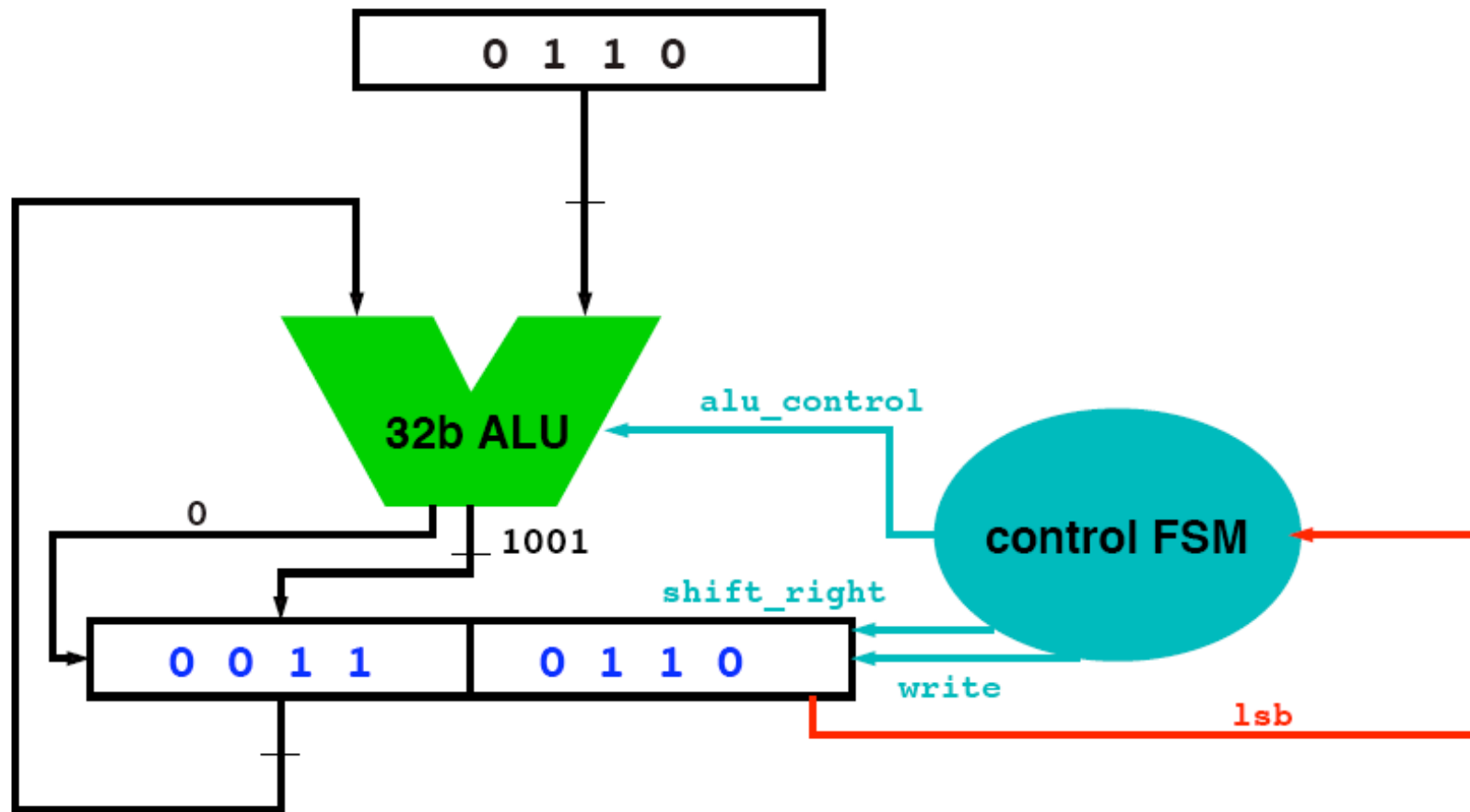

# Integer Multiplication

---

- Each step requires an add and shift
- MIPS: `hi` and `lo` registers correspond to the two parts of the product register
- Hardware implements `multu`
- Signed multiplication:
  - Determine sign of the inputs, make inputs positive
  - Use `multu` hardware, fix up sign
  - Better: Booth's algorithm

