

CS 316: Logic and State

Kavita Bala

Fall 2007


Computer Science

Cornell University



Stateful Components

- Until now is combinatorial logic
 - Output is computed when inputs are present
 - System has no internal state
 - Nothing computed in the present can depend on what happened in the past!
- Need a way to record data
- Need a way to build stateful circuits
- Need a state-holding device

Bistable Devices

 


- In stable state, $\bar{A} = B$

  

- How do we change the state?

Kavita Bala, Computer Science, Cornell University

SR Latch

 


S	R	Q	\bar{Q}
0	0	Q	\bar{Q}
0	1	0	1
1	0	1	0
1	1	?	?

- Set-Reset (S-R) Latch
- Q: Stored value and its complement
- S=1 and R=1 ?

Kavita Bala, Computer Science, Cornell University

D Latch

 


- Data Latch
 - Easier to use than an SR latch
 - No possibility of entering an undefined state
- When D changes, Q changes
 - ... immediately
- Need to control when the output changes

Kavita Bala, Computer Science, Cornell University



Clocks

 - Clocks help with modifying the contents of state-holding elements
- A free running signal
 - Generated by an oscillating crystal
- Clock signal has a fixed cycle time (aka cycle period)
- Clock frequency = $1/\text{cycle time}$



Kavita Bala, Computer Science, Cornell University

Edge-triggering

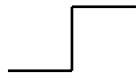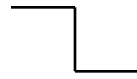
- Can design circuits to change on the rising or falling edge
- Trigger on rising edge = positive edge-triggered 
- Trigger on falling edge = negative edge-triggered 
- Inputs must be stable just before the triggering edge



Kavita Bala, Computer Science, Cornell University


First Attempt

- How does the output behave?

 


Kavita Bala, Computer Science, Cornell University

First Attempt

 


- How does the output behave?

 


Kavita Bala, Computer Science, Cornell University

First Attempt

 


 - How does the output behave?
- Changes in D that occur when the clock is low are deferred until clock high
- Changes when clock is high are registered immediately



Kavita Bala, Computer Science, Cornell University


Master-Slave Flip-Flop

 


- Outputs change only on falling edges
- Data is captured on rising edges
- 1 cycle delay
 - but works out perfectly – data for the next stage is ready 1 cycle ahead of time

Kavita Bala, Computer Science, Cornell University

Registers

 


 - A register is simply a set of master-slave flip-flops in parallel with a shared clock



Kavita Bala, Computer Science, Cornell University


Keyboard

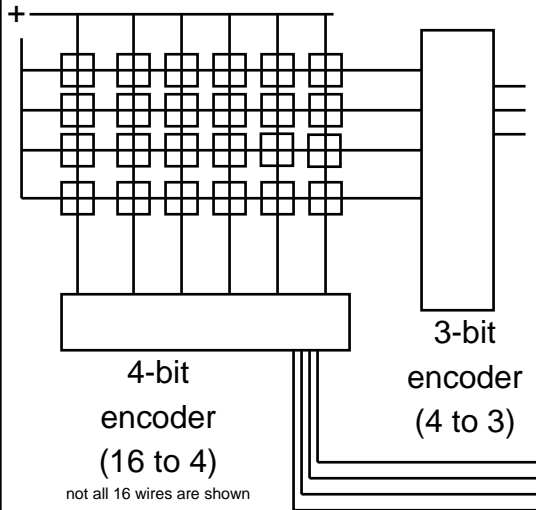

- When a key is pressed
 - Compute a 7-bit key identifier
- Store this keycode
 - The computer may not be ready to read it right away

Kavita Bala, Computer Science, Cornell University

Keyboard with Last Key Display

 

Kavita Bala, Computer Science, Cornell University

Summary

- We can now build interesting devices with sensors
 - Using combinatorial logic
- We can also store data values
 - In state-holding elements
 - Coupled with clocks

Kavita Bala, Computer Science, Cornell University

Finite State Machines

Finite State Machines

- An electronic machine which has
 - external inputs
 - externally visible outputs
 - internal state
- Output and next state depend on
 - inputs
 - current state


Kavita Bala, Computer Science, Cornell University

Designing a FSM

- Draw a state diagram
- Write down state transition table
- Assign numbers to states
- Determine logic equations for all flip-flops and outputs

Kavita Bala, Computer Science, Cornell University

A Simple Example

 

- Goal: flash hello on LEDs
- Inputs: clock
- Outputs: Just one 7-segment LED

- Flash “h” then “e” then “l” then “l” then “o”

– h = $\langle 0011101 \rangle$


– e = $\langle 0111110 \rangle$

– l = $\langle 0010110 \rangle$

– o = $\langle 1110111 \rangle$

Kavita Bala, Computer Science, Cornell University

HELLObox: State Diagram

 

- Determine the transitions
 - label all edges (transitions) with the inputs that cause them, unlabeled edges are unconditional transitions
 - show start state

Kavita Bala, Computer Science, Cornell University

HELLObox: State Table

- Build state table
 - rote encoding of the state diagram

Current State	Next State	Output
S0	S1	0011101
S1	S2	0111110
S2	S3	0010110
S3	S4	0010110
S4	S0	1110111

Kavita Bala, Computer Science, Cornell University


HELLObox: State Assignment 1

- Assign bit patterns to states
 - Try to make resulting device simple
 - One option is shown
- Determine logic equations for
 - every bit of output
 - next state
 - for every flip-flop and output

Current State	Next State	Output
000	001	0011101
001	010	0111110
010	011	0010110
011	100	0010110
100	000	1110111

Kavita Bala, Computer Science, Cornell University

HELLObox #1

 

- 12 bits of information (7 outputs + 3 bits of next state) are computed by the combinational circuit
- All 10 bits have non-trivial logic equations

Kavita Bala, Computer Science, Cornell University


HELLObox: State Assignment 2

- Assign bit patterns to states to make the resulting device simple
- Here, we use far more bits than necessary
 - to simplify the combinational circuit

Current State	Next State	Output
00111010	01111100	0011101
01111100	00101100	0111110
00101100	00101101	0010110
00101101	11101110	0010110
11101110	00111010	1110111


Kavita Bala, Computer Science, Cornell University

HELLObox #2

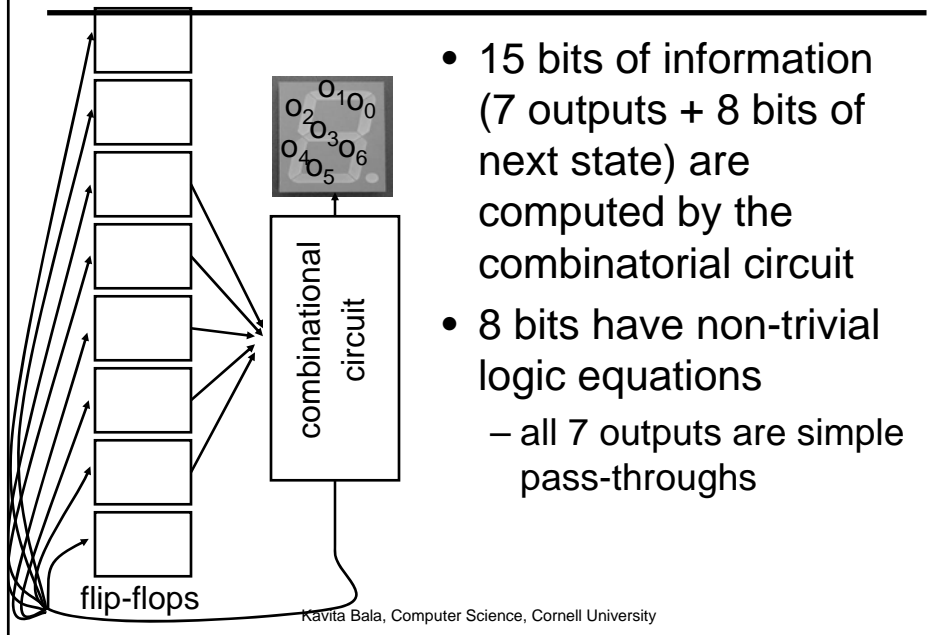


FSM: Serial Adder

 - Add two input bit streams
 - streams are sent with least-significant-bit (lsb) first



Kavita Bala, Computer Science, Cornell University

FSM: State Diagram

 

- Two states: S0 (no carry), S1 (carry in hand)
- Inputs: a and b
- Output: z
 - Arcs labelled with input bits a and b, and output z

Kavita Bala, Computer Science, Cornell University

Serial Adder: State Table

a	b	state	z	next state
0	0	S0	0	S0
0	1	S0	1	S0
1	0	S0	1	S0
1	1	S0	0	S1
0	0	S1	1	S0
0	1	S1	0	S1
1	0	S1	0	S1
1	1	S1	1	S1

- Write down all input and state combinations

Kavita Bala, Computer Science, Cornell University


Serial Adder: State Assignment

a	b	s	z	s'
0	0	0	0	0
0	1	0	1	0
1	0	0	1	0
1	1	0	0	1
0	0	1	1	0
0	1	1	0	1
1	0	1	0	1
1	1	1	1	1

- Two states, so 1-bit is sufficient
 - A single flip-flop will encode the state

Kavita Bala, Computer Science, Cornell University

Serial Adder: Circuit

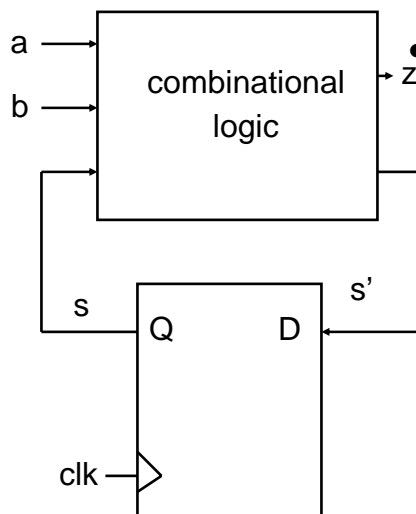

Equations

$$- z = \bar{a}\bar{b}s + \bar{a}b\bar{s} + a\bar{b}\bar{s} + abs$$

$$- s' = \bar{a}bs + \bar{a}b\bar{s} + a\bar{b}\bar{s} + abs$$

Kavita Bala, Computer Science, Cornell University