

Gates and Logic: From Transistors to Logic Gates and Logic Circuits

Prof. Anne Bracy

CS 3410

Computer Science

Cornell University

The slides are the product of many rounds of teaching CS 3410 by Professors Weatherspoon, Bala, Bracy, and Sireer.


Goals for Today

- From Switches to Logic Gates to Logic Circuits
- Transistors, Logic Gates, Truth Tables
- Logic Circuits
 - Identity Laws
 - From Truth Tables to Circuits (Sum of Products)
- Logic Circuit Minimization
 - Algebraic Manipulations
 - Karnaugh Maps


Silicon Valley & the Semiconductor Industry

- Transistors:
- Youtube video “How does a transistor work”
<https://www.youtube.com/watch?v=lcrBqCFLHIY>
- Break: show some Transistor, Fab, Wafer photos

Transistors 101

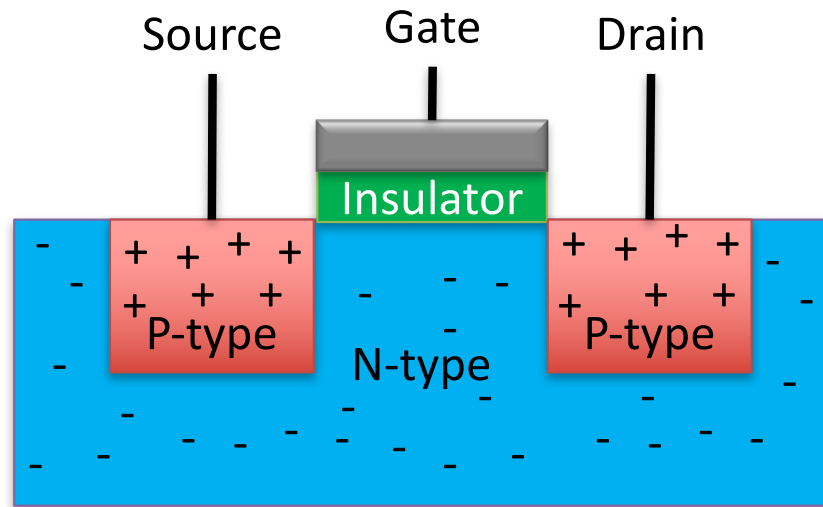

Off

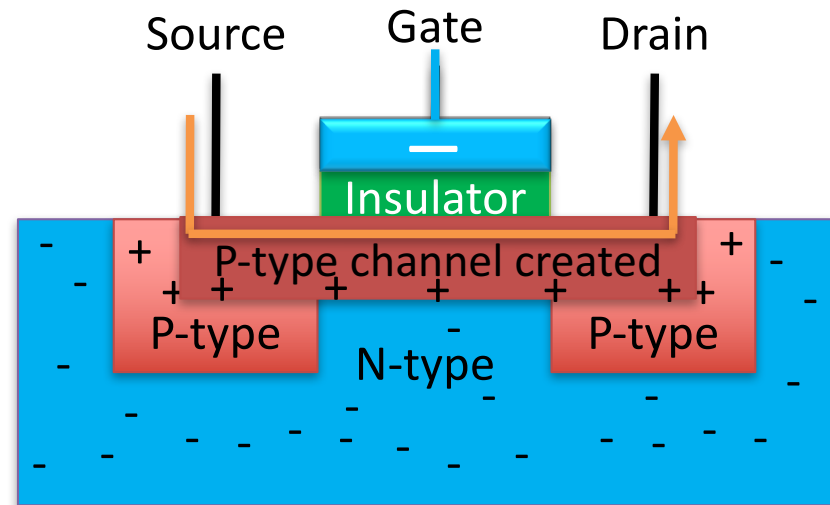

On

N-Type Silicon: negative free-carriers (electrons)

P-Type Silicon: positive free-carriers (holes)

P-Transistor: negative charge on gate generates electric field that creates a (+ charged) p-channel connecting source & drain


N-Transistor: works the opposite way

Metal-Oxide Semiconductor (Gate-Insulator-Silicon)


- Complementary MOS = **CMOS** technology uses both p- & n-type transistors

CMOS Notation


N-type

 


Off/Open

 


On/Closed

 


P-type

 

Off/Open

 

On/Closed

 

Gate input controls whether current can flow between the other two terminals or not.

Hint: the "o" bubble of the p-type tells you that this gate wants a 0 to be turned on

iClicker Question


Which of the following statements is **false**?

- (A) P- and N-type transistors are both used in CMOS designs.
- (B) As transistors get smaller, the frequency of your processor will keep getting faster.
- (C) As transistors get smaller, you can fit more and more of them on a single chip.
- (D) Pure silicon is a semi conductor.
- (E) Experts believe that Moore's Law will soon end.


2-Transistor Combination: NOT

- Logic gates are constructed by combining transistors in complementary arrangements
- Combine p&n transistors to make a NOT gate:

CMOS Inverter :

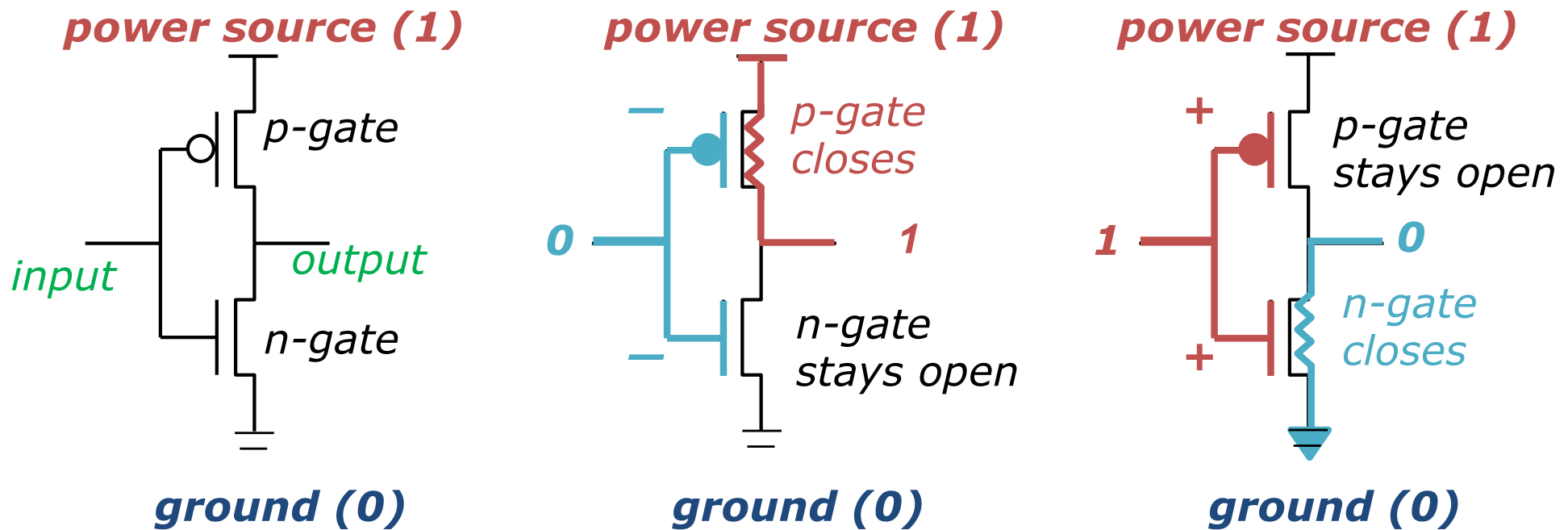


Inverter

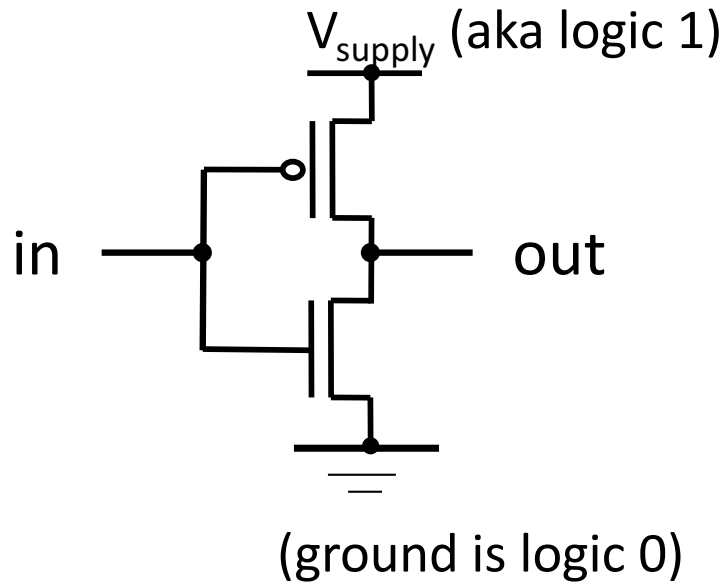

Function: NOT

Symbol:

 

Truth Table:

| In | Out |
|----|-----|
| 0 | 1 |
| 1 | 0 |

Logic Gates

- Digital circuit that either allows signal to pass through it or not
- Used to build logic functions
- Seven basic logic gates:

AND

OR

NOT,

NAND (not AND),

NOR (not OR),

XOR

XNOR (not XOR)




George Boole, (1815–1864)

Did you know?

George Boole Inventor of the idea of logic gates. He was born in Lincoln, England and he was the son of a shoemaker.


Logic Gates: Names, Symbols, Truth Tables

NOT:

 


| A | Out |
|---|-----|
| 0 | 1 |
| 1 | 0 |

AND:

 


| A | B | Out |
|---|---|-----|
| 0 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

NAND:

 


| A | B | Out |
|---|---|-----|
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

OR:

 


| A | B | Out |
|---|---|-----|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 1 |

NOR:

 


| A | B | Out |
|---|---|-----|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 0 |

XOR:

 


| A | B | Out |
|---|---|-----|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

XNOR:

 


| A | B | Out |
|---|---|-----|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

NOR Gate

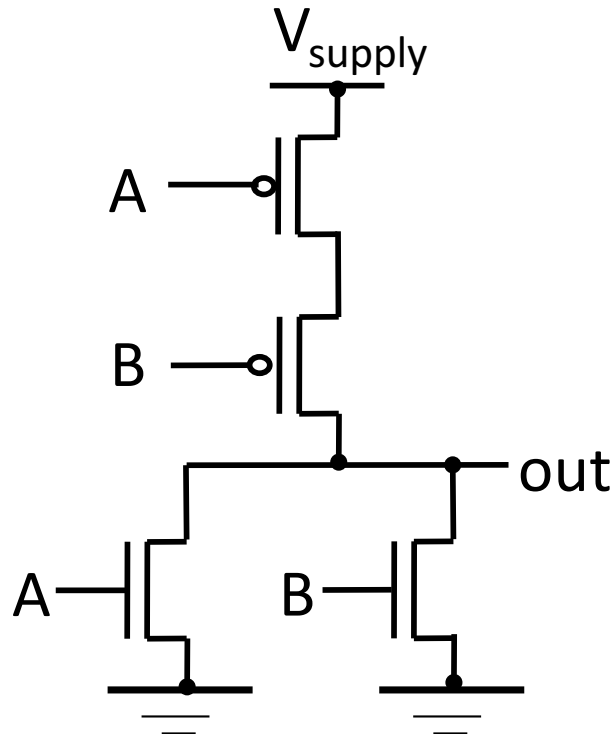

Function: NOR

Symbol:

 


Truth Table:

| A | B | out |
|---|---|-----|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 0 |

iClicker Question

Which Gate is this?

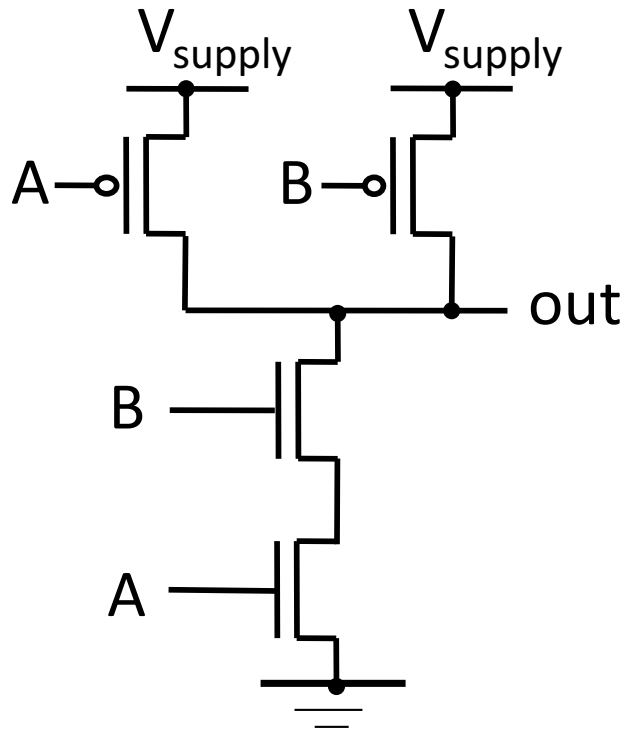






Function:

Symbol:





Truth Table:

| A | B | out |
|---|---|-----|
| 0 | 0 | |
| 0 | 1 | |
| 1 | 0 | |
| 1 | 1 | |

    - (A) NOT 
- (B) OR 
- (C) XOR 
- (D) AND 
- (E) NAND 


Abstraction

- Hide complexity through simple abstractions
 - **Simplicity**
 - Box diagram represents inputs and outputs
 - **Complexity**
 - Hides underlying NMOS- and PMOS-transistors and atomic interactions



iClicker Question

Which Gate is this?

 






Function:

Symbol:

Truth Table:



| A | B | out |
|---|---|-----|
| 0 | 0 | |
| 0 | 1 | |
| 1 | 0 | |
| 1 | 1 | |

- (A) NOT 
- (B) OR 
- (C) XOR 
- (D) AND 
- (E) NAND 



Universal Gates

- NAND and NOR:
 - Can implement *any* function with NAND or just NOR gates
 - useful for manufacturing



- NOT:

  


- AND:

  

- OR:

  

What does this logic circuit do?

 

Function:

Symbol:

Truth Table:

| a | b | d | Out |
|---|---|---|-----|
| 0 | 0 | 0 | |
| 0 | 0 | 1 | |
| 0 | 1 | 0 | |
| 0 | 1 | 1 | |
| 1 | 0 | 0 | |
| 1 | 0 | 1 | |
| 1 | 1 | 0 | |
| 1 | 1 | 1 | |



Multiplexing Like a Boss

Goals for Today

- From Switches to Logic Gates to Logic Circuits
- Transistors, Logic Gates, Truth Tables
- Logic Circuits
 - From Truth Tables to Circuits (Sum of Products)
 - **Identity Laws**
- Logic Circuit Minimization
 - Algebraic Manipulations
 - Karnaugh Maps

Logic Implementation

How to implement a desired logic function?


| a | b | c | out | minterm |
|---|---|---|-----|---------------------------|
| 0 | 0 | 0 | 0 | $\bar{a} \bar{b} \bar{c}$ |
| 0 | 0 | 1 | 1 | $\bar{a} \bar{b} c$ |
| 0 | 1 | 0 | 0 | $\bar{a} b \bar{c}$ |
| 0 | 1 | 1 | 1 | $\bar{a} b c$ |
| 1 | 0 | 0 | 0 | $a \bar{b} \bar{c}$ |
| 1 | 0 | 1 | 1 | $a \bar{b} c$ |
| 1 | 1 | 0 | 0 | $a b \bar{c}$ |
| 1 | 1 | 1 | 0 | $a b c$ |

1) Write **minterms**

 2) Write **sum of products**:

OR of all minterms where out=1

$$\text{out} = \bar{a}\bar{b}c + \bar{a}bc + a\bar{b}c$$



Any combinational circuit can be implemented in two levels of logic (ignoring inverters)

Logic Equations

NOT: $= \bar{a}$ $= !a$ $= \neg a$

AND: $= a \cdot b$ $= a \& b$ $= a \wedge b$

OR: $= a + b$ $= a | b$ $= a \vee b$

XOR: $= a \oplus b = \underline{a}b + \bar{a}\bar{b}$

NAND:

$$\overline{(a \bullet b)} = !(a \& b) = \neg (a \wedge b)$$

NOR:

$$\overline{(a + b)} = !(a | b) = \neg (a \vee b)$$

XNOR:

$$\overline{(a \oplus b)} = \overline{a\bar{b} + \bar{a}b}$$

Logic Equations

- Constants: true = 1, false = 0
- Variables: a, b, out, ...
- Operators (above): AND, OR, NOT, etc.

Identities

Identities useful for manipulating logic equations

- For optimization & ease of implementation

$$a + 0 = a$$

$$a + 1 = 1$$

$$a + \bar{a} = 1$$

$$a \cdot 0 = 0$$

$$a \cdot 1 = a$$

$$a \cdot \bar{a} = 0$$

Identities

Identities useful for manipulating logic equations

- For optimization & ease of implementation


$$\overline{(a + b)} = \bar{a} \bullet \bar{b}$$

$$\overline{(ab)} = \bar{a} + \bar{b}$$

$$a + ab = a$$

$$a(b+c) = ab + ac$$
 
$$\overline{a(b + c)} = \bar{a} + \bar{b} \bullet \bar{c}$$



Goals for Today

- From Switches to Logic Gates to Logic Circuits
- Transistors, Logic Gates, Truth Tables
- Logic Circuits
 - Identity Laws
 - From Truth Tables to Circuits (Sum of Products)
- **Logic Circuit Minimization – *why?***
 - Algebraic Manipulations
 - Karnaugh Maps

Minimization Example

$$a + 0 = a$$

$$a + 1 = 1$$

$$a + \bar{a} = 1$$

$$a \cdot 0 = 0$$

$$a \cdot 1 = a$$

$$a \cdot \bar{a} = 0$$

$$a + a b = a$$

$$a(b+c) = ab + ac$$

$$\overline{(a + b)} = \bar{a} \bullet \bar{b}$$

$$\overline{(ab)} = \bar{a} + \bar{b}$$

$$\overline{a(b + c)} = \bar{a} + \bar{b} \bullet \bar{c}$$

Minimize this logic equation:

$$\begin{aligned}(a+b)(a+c) &= (a+b)a + (a+b)c \\ &= aa + ba + ac + bc \\ &= a + a(b+c) + bc \\ &= a + bc\end{aligned}$$

iClicker Question

$$a + 0 = a$$

$$a + 1 = 1$$

$$a + \bar{a} = 1$$

$$a \cdot 0 = 0$$

$$a \cdot 1 = a$$

$$a \cdot \bar{a} = 0$$

$$a + a b = a$$

$$a(b+c) = ab + ac$$

$$\overline{(a + b)} = \bar{a} \bullet \bar{b}$$

$$\overline{(ab)} = \bar{a} + \bar{b}$$

$$\overline{a(b + c)} = \bar{a} + \bar{b} \bullet \bar{c}$$

$$(a+b)(a+c) \rightarrow a + bc$$

How many gates were required before and after?

BEFORE

AFTER

(A) 2 OR

1 OR

(B) 2 OR, 1 AND

2 OR

(C) 2 OR, 1 AND

1 OR, 1 AND

(D) 2 OR, 2 AND

2 OR

(E) 2 OR, 2 AND

2 OR, 1 AND

Checking Equality w/Truth Tables

circuits \leftrightarrow truth tables \leftrightarrow equations

Example: $(a+b)(a+c) = a + bc$

| a | b | c | (a+b) | LHS | (a+c) | RHS | bc |
|---|---|---|-------|-----|-------|-----|----|
| 0 | 0 | 0 | | | | | |
| 0 | 0 | 1 | | | | | |
| 0 | 1 | 0 | | | | | |
| 0 | 1 | 1 | | | | | |
| 1 | 0 | 0 | | | | | |
| 1 | 0 | 1 | | | | | |
| 1 | 1 | 0 | | | | | |
| 1 | 1 | 1 | | | | | |

Checking Equality w/Truth Tables

circuits \leftrightarrow truth tables \leftrightarrow equations

Example: $(a+b)(a+c) = a + bc$

| a | b | c | $(a+b)$ | LHS | $(a+c)$ | RHS | bc |
|---|---|---|---------|-----|---------|-----|------|
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 0 | 1 | 0 | 0 |
| 0 | 1 | 0 | 1 | 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 | 1 | 1 | 1 | 0 |
| 1 | 0 | 1 | 1 | 1 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 1 | 1 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |

Minimization in Practice

How does one find the most efficient equation?

- Manipulate algebraically until...?
- Use **Karnaugh Maps** (optimize visually)
- Use a software optimizer

For large circuits

- Decomposition & reuse of building blocks

Building a Karnaugh Map

| a | b | c | out |
|---|---|---|-----|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 0 |

Sum of minterms yields

out =

$$\bar{a}\bar{b}c + \bar{a}bc + a\bar{b}\bar{c} + abc$$

| | | ab | | | |
|---|---|----|----|----|----|
| | | 00 | 01 | 11 | 10 |
| c | 0 | 0 | 0 | 0 | 1 |
| | 1 | 1 | 1 | 0 | 1 |

K-maps identify which inputs are relevant to the output

Minimization with K-Maps

| | | | | |
|---|----|----|----|----|
| | ab | | | |
| c | 00 | 01 | 11 | 10 |
| 0 | 0 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 | 1 |

(1) Circle the 1's (see below)

(2) Each circle is a logical component of the final equation

$$= a\bar{b} + \bar{a}c$$

Rules:

- Use fewest circles necessary to cover all 1's
- Circles must cover *only* 1's
- Circles span rectangles of size power of 2 (1, 2, 4, 8...)
- Circles should be as large as possible (all circles of 1?)
- Circles may wrap around edges of K-Map
- 1 may be circled multiple times *if* that means fewer circles

Karnaugh Minimization Tricks (1)

| c \ ab | 00 | 01 | 11 | 10 |
|--------|----|----|----|----|
| 0 | 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 | 0 |

Minterms can overlap

$$\text{out} = b\bar{c} + a\bar{c} + ab$$

| c \ ab | 00 | 01 | 11 | 10 |
|--------|----|----|----|----|
| 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 | 0 |

Minterms can span 2, 4, 8 or more cells

$$\text{out} = \bar{c} + ab$$

Karnaugh Minimization Tricks (2)

| cd \ ab | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| 00 | 0 | 0 | 0 | 0 |
| 01 | 1 | 0 | 0 | 1 |
| 11 | 1 | 0 | 0 | 1 |
| 10 | 0 | 0 | 0 | 0 |

- The map wraps around
 $out = \bar{b}d$

| cd \ ab | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| 00 | 1 | 0 | 0 | 1 |
| 01 | 0 | 0 | 0 | 0 |
| 11 | 0 | 0 | 0 | 0 |
| 10 | 1 | 0 | 0 | 1 |

$$out = \bar{b} \bar{d}$$

Don't Cares

| cd \ ab | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| 00 | 0 | 0 | 0 | 0 |
| 01 | 1 | x | x | x |
| 11 | 1 | x | x | 1 |
| 10 | 0 | 0 | 0 | 0 |

| cd \ ab | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| 00 | 1 | 0 | 0 | x |
| 01 | 0 | x | x | 0 |
| 11 | 0 | x | x | 0 |
| 10 | 1 | 0 | 0 | 1 |

“Don’t care” values can be interpreted individually in whatever way is convenient

- assume all x’s = 1

→ out = d

- assume middle x’s = 0 (ignore them)

- assume 4th column x = 1

→ out = $\bar{b} \bar{d}$

Takeaway

- Binary —two symbols: **true** and **false**—is the basis of Logic Design
- More than one Logic Circuit can implement same Logic function. Use Algebra (Identities) or Truth Tables to show equivalence.
- Any logic function can be implemented as “sum of products”. Karnaugh Maps minimize number of gates.

Summary

- Most modern devices made of billions of transistors
 - You will build a processor in this course!
 - Modern transistors made from semiconductor materials
 - Transistors used to make logic gates and logic circuits
- We can now implement any logic circuit
 - Use P- & N-transistors to implement NAND/NOR gates
 - Use NAND or NOR gates to implement the logic circuit
 - *Efficiently*: use K-maps to find required minimal terms