

State

CS 3410

Computer Science


Cornell University

[K. Bala, A. Bracy, E. Simer, and H. Weatherspoon]

Stateful Components

Combinational logic

 
- Output computed directly from inputs
- System has no internal state
- Nothing depends on the past!



Need:

- to record data
- to build stateful circuits
- a state-holding device

State Examples: Program Memory & PC

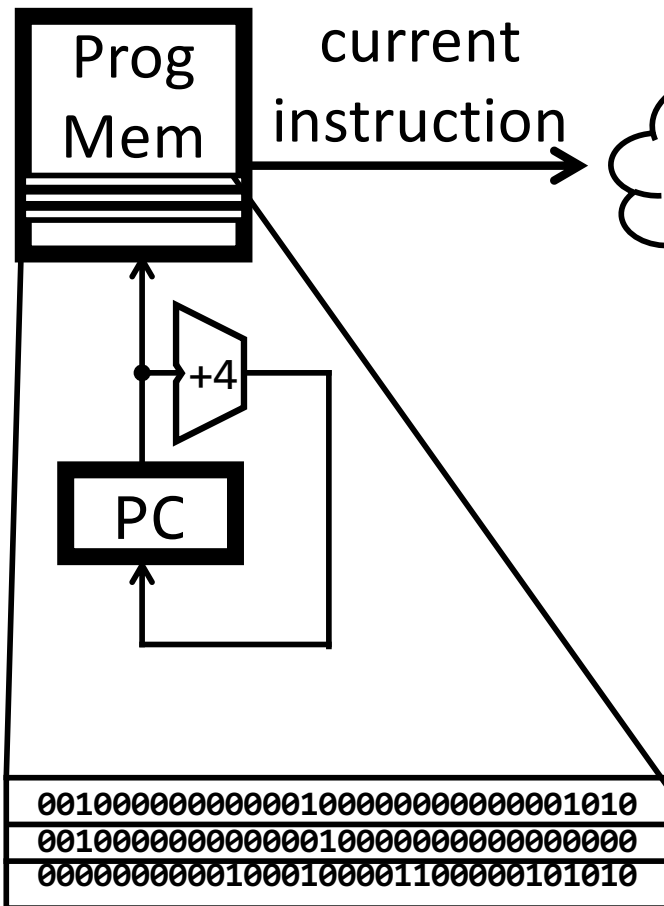

A basic processor

- fetches
- decodes
- executes

one instruction at a time

Instructions live in **Program Memory**

PC = Program Counter, address of current instruction

“Next Instruction Address” = $PC + 4$


When should we update the PC?

As fast and as often as possible?

Clocks

Clock helps coordinate state changes

 
- Fixed period
- Frequency = $1/\text{period}$




Edge Triggered State Changes

State changes at clock edge

positive edge-triggered

 


negative edge-triggered

 

Need to design edge-triggered storage

Positive edge-triggered D Flip-Flop:

 - Data captured when clock low
- Output changes only on rising edge
(could also design it to be negative edge-triggered)




Clock Methodology


Signals must be stable prior to rising edge

Positive edge-triggered D Flip-Flop:

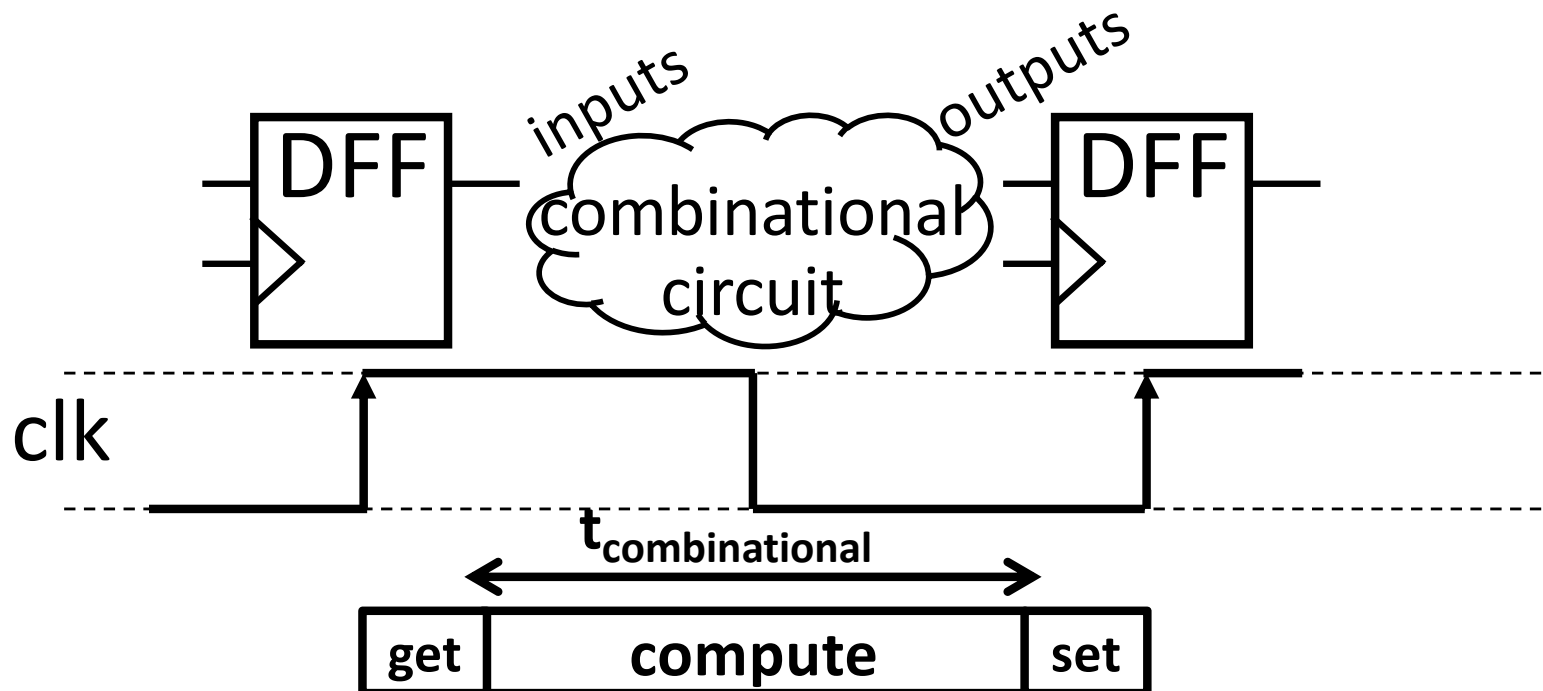- Output changes only on rising edge
- Data captured when clock low




State Examples: Program Memory & PC

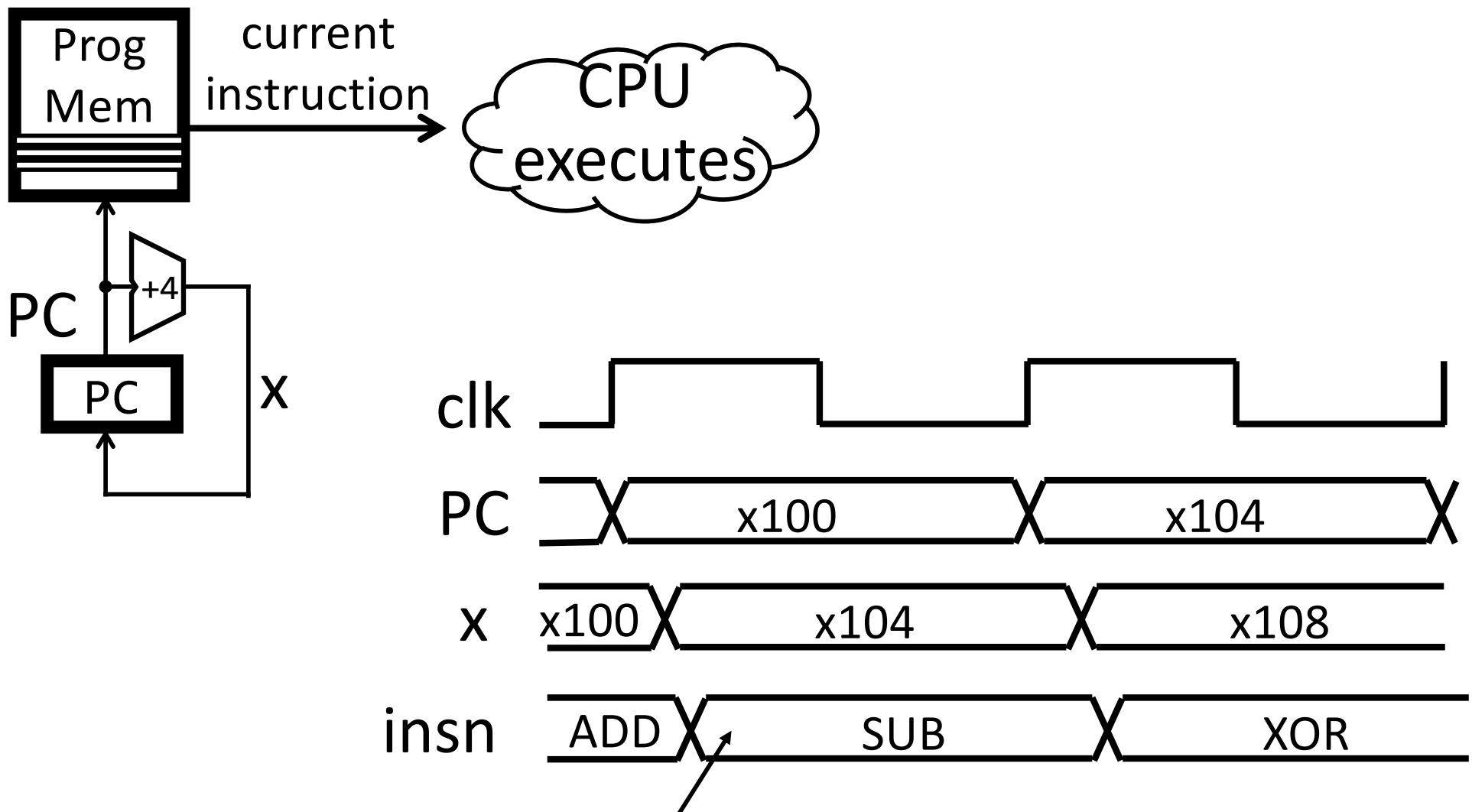

(a 32 bit encoding of a subtract instruction)

iClicker Question

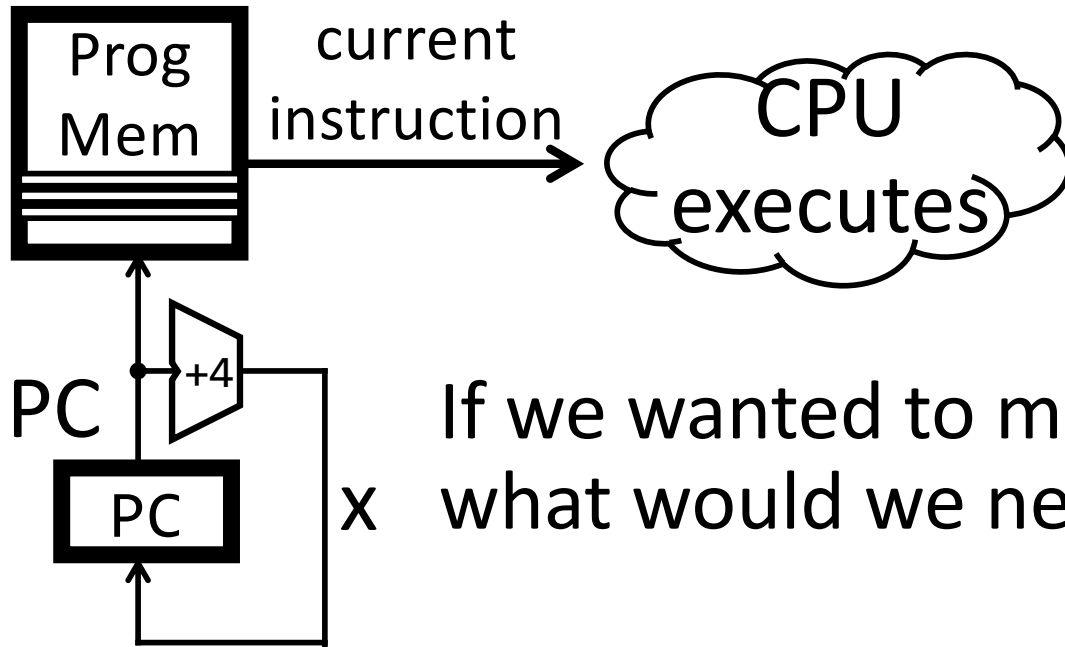

If we wanted to make the clock faster, what would we need to speed up?

- (A) the +4 adder
- (B) the time it takes to read Program Memory
- (C) the time it takes to execute an instruction
- (D) B or C
- (E) A, B & C


Goals for Today

Clocks


State

- Storing 1 bit
- Storing N bits:
 - Registers
 - Memory

Registers

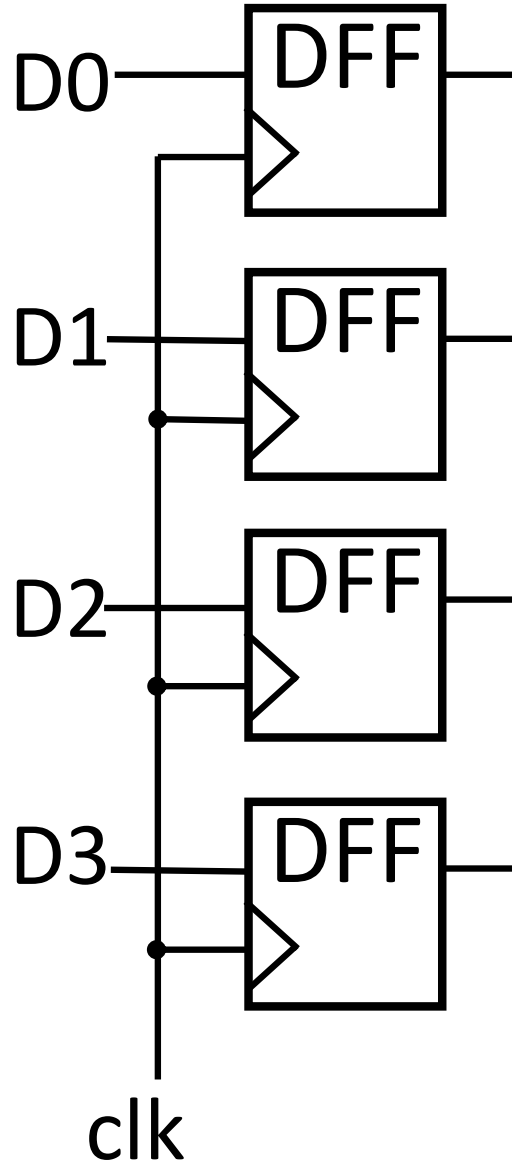

 
- D flip-flops in parallel
- shared clock
- Additional (optional) inputs: writeEnable, reset, ...



Register File

Register File

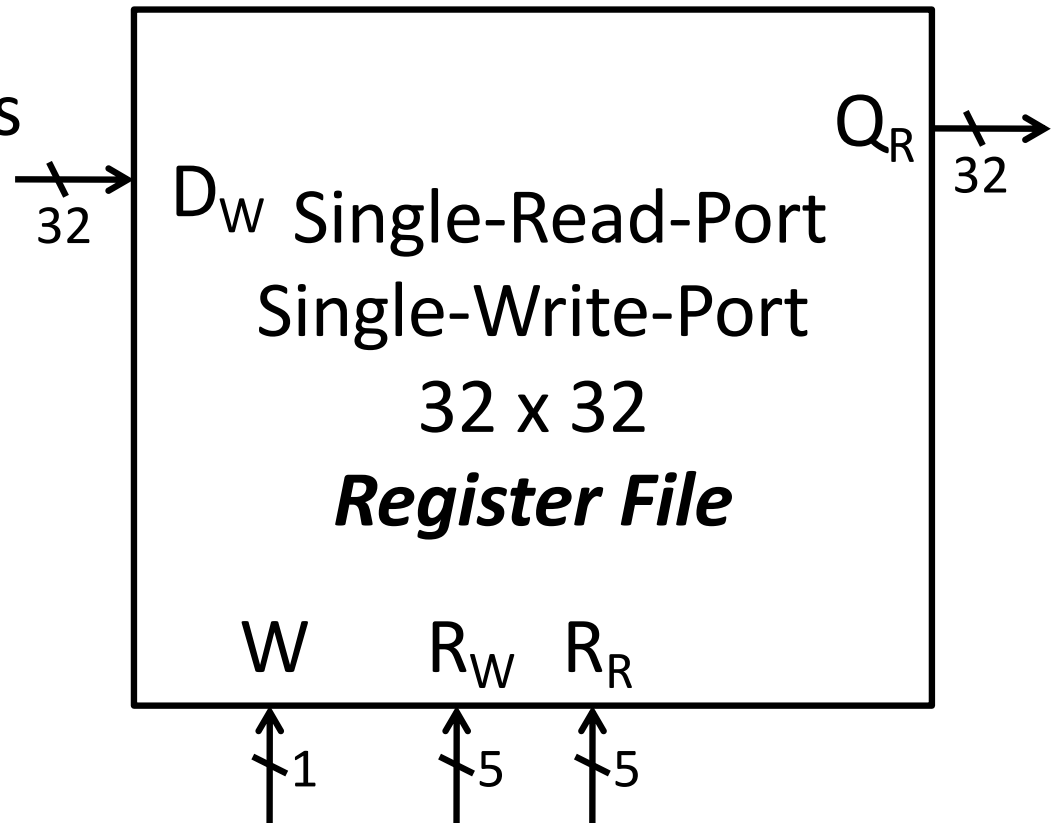
- N read/write registers
- Indexed by register number



Writing to the Register File (1)

Register File

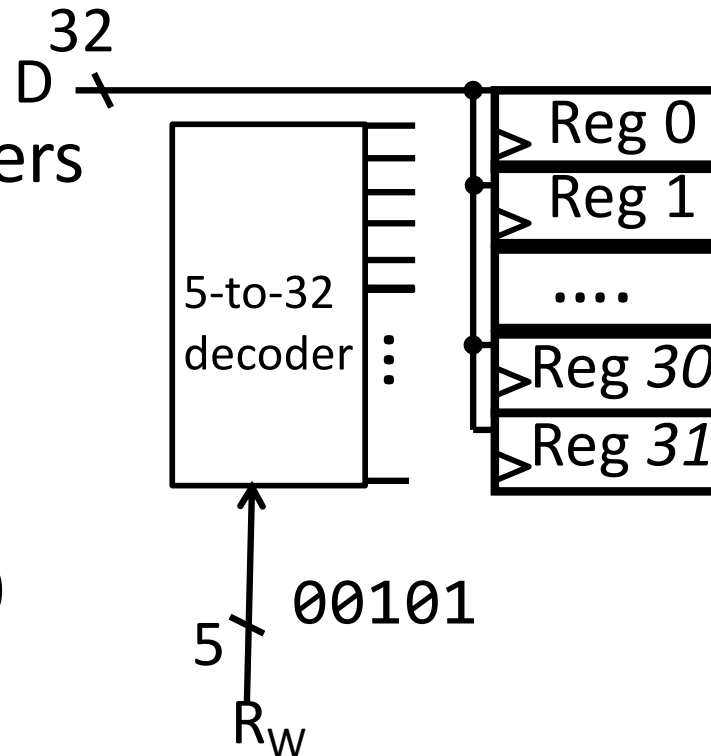- N read/write registers
- Indexed by register number




```
addi r5, r0, 10
```

How to write to **one** register in the register file?

- Need a decoder




Aside: 3-to-8 decoder truth table & circuit

i2	i1	i0	o0	o1	o2	o3	o4	o5	o6	o7
0	0	0								
0	0	1								
0	1	0								
0	1	1								
1	0	0								
1	0	1								
1	1	0								
1	1	1								

 

Aside: 3-to-8 decoder truth table & circuit

i2	i1	i0	o0	o1	o2	o3	o4	o5	o6	o7
0	0	0	1							
0	0	1		1						
0	1	0			1					
0	1	1				1				
1	0	0					1			
1	0	1						1		
1	1	0							1	
1	1	1								1

   


Writing to the Register File (2)

Register File

- N read/write registers
- Indexed by register number

```
addi r5, r0, 10
```

 


How to write to **one** register in the register file?

- Need a decoder
- Write enable signal prevents unintended writes

Reading from the Register File

Register File

 - N read/write registers
- Indexed by register number




How to read from one register? Need:

- (A) Encoder
- (B) Decoder
- (C) Or Gate
- (D) Multiplexor

Reading from the Register File

Register File

 - N read/write registers
- Indexed by register number



How to read from one register?

- Need a multiplexor


Reading from the Register File

Register File

- N read/write registers
- Indexed by register number

How to read from two registers?

- Need 2 multiplexors!

 


Complete Register File

Register File

- N read/write registers
- Indexed by register number

Implementation:

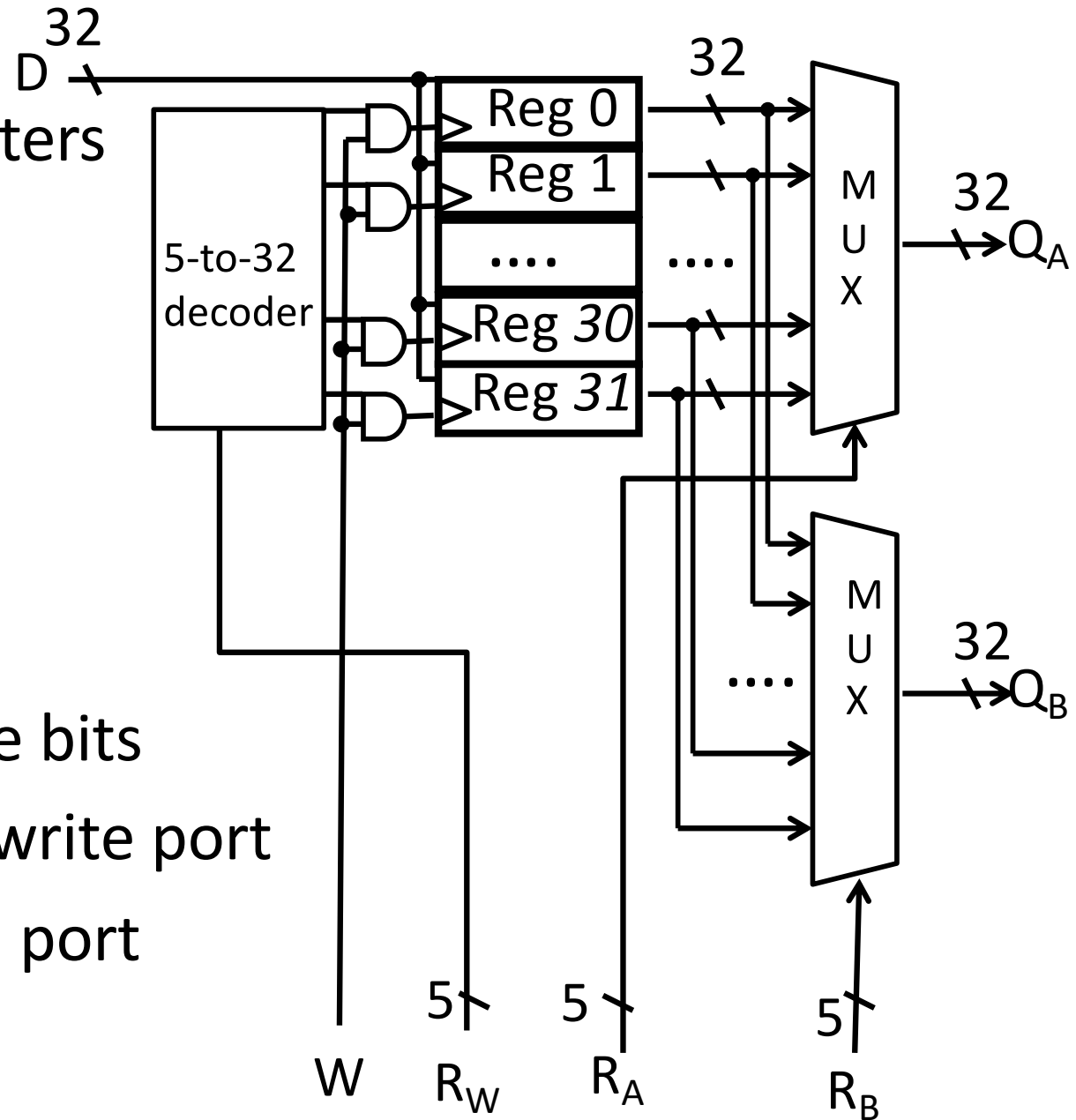
- D flip flops to store bits
- Decoder for each write port
- Mux for each read port



Register File

Register File

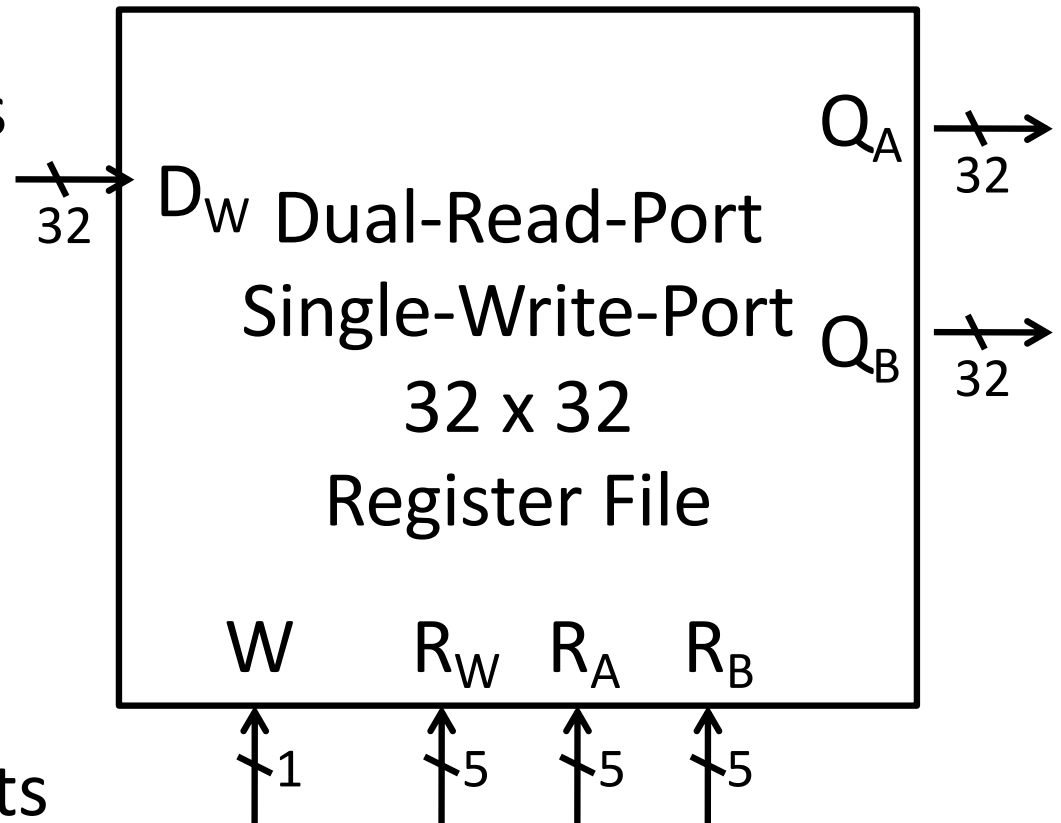- N read/write registers
- Indexed by register number




Implementation:

- D flip flops to store bits
- Decoder for each write port
- Mux for each read port

MIPS Register file

MIPS register file

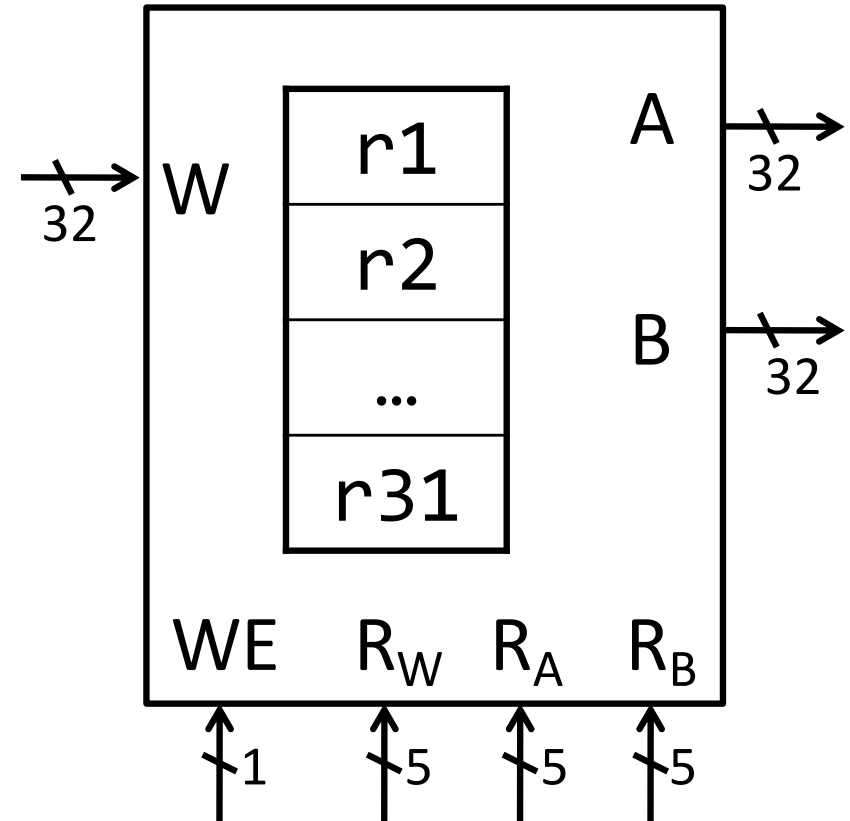- 32 x 32-bit registers
- r0 wired to zero
- Write port indexed via R_W
 - on falling edge when $WE=1$
- Read ports indexed via R_A, R_B




Registers

- Numbered from 0 to 31.
- Can be referred by number: \$0, \$1, \$2, ... \$31
- Convention, each register also has a name:
 - \$16 - \$23 → \$s0 - \$s7, \$8 - \$15 → \$t0 - \$t7

iClicker Question

If we wanted to support 64 registers, what would change?

 
- (A) W, A, B $32 \rightarrow 64$
- (B) R_w, R_a, R_b $5 \rightarrow 6$
- (C) W $32 \rightarrow 64$, R_w $5 \rightarrow 6$
- (D) A & B only



Tradeoffs

Register File tradeoffs

 - + Very fast (a few gate delays for both read and write)
 - + Adding extra ports is straightforward
 - Doesn't scale
- e.g. 32Mb register file with 32 bit registers (1M registers)
Need 32x 1M-to-1 multiplexor and 32x 20-to-1M decoder
How many logic gates/transistors?



Goals for Today


Clocks

State

- Storing 1 bit
- Storing N bits:
 - Registers
 - Memory

Memory

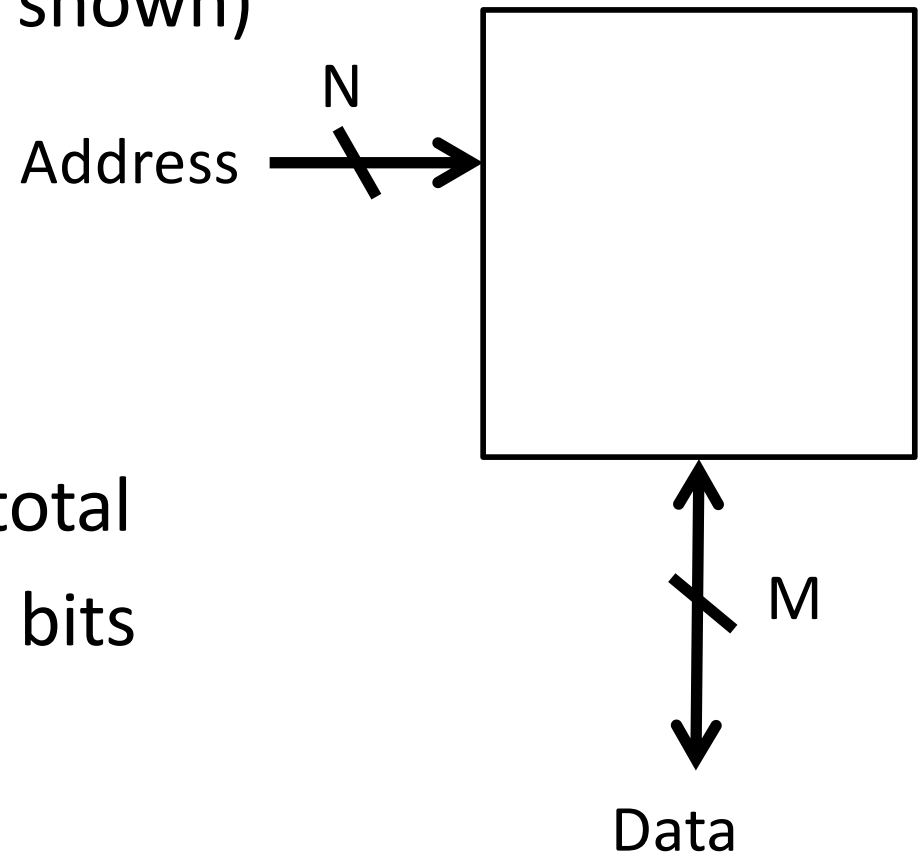- Storage Cells + bus
- Inputs: Address, Data (for writes)
- Outputs: Data (for reads)
- Also need R/W signal (not shown)




- N address bits $\rightarrow 2^N$ words total
- M data bits \rightarrow each word M bits

Memory

- Storage Cells + bus
- Decoder selects a word line
- R/W selector determines access type
- Word line is then coupled to the data lines

 
note: w/ a tri-state buffer, not a huge mux!



4x2 Memory

E.g. How do we design
a 4 x 2 Memory Module?

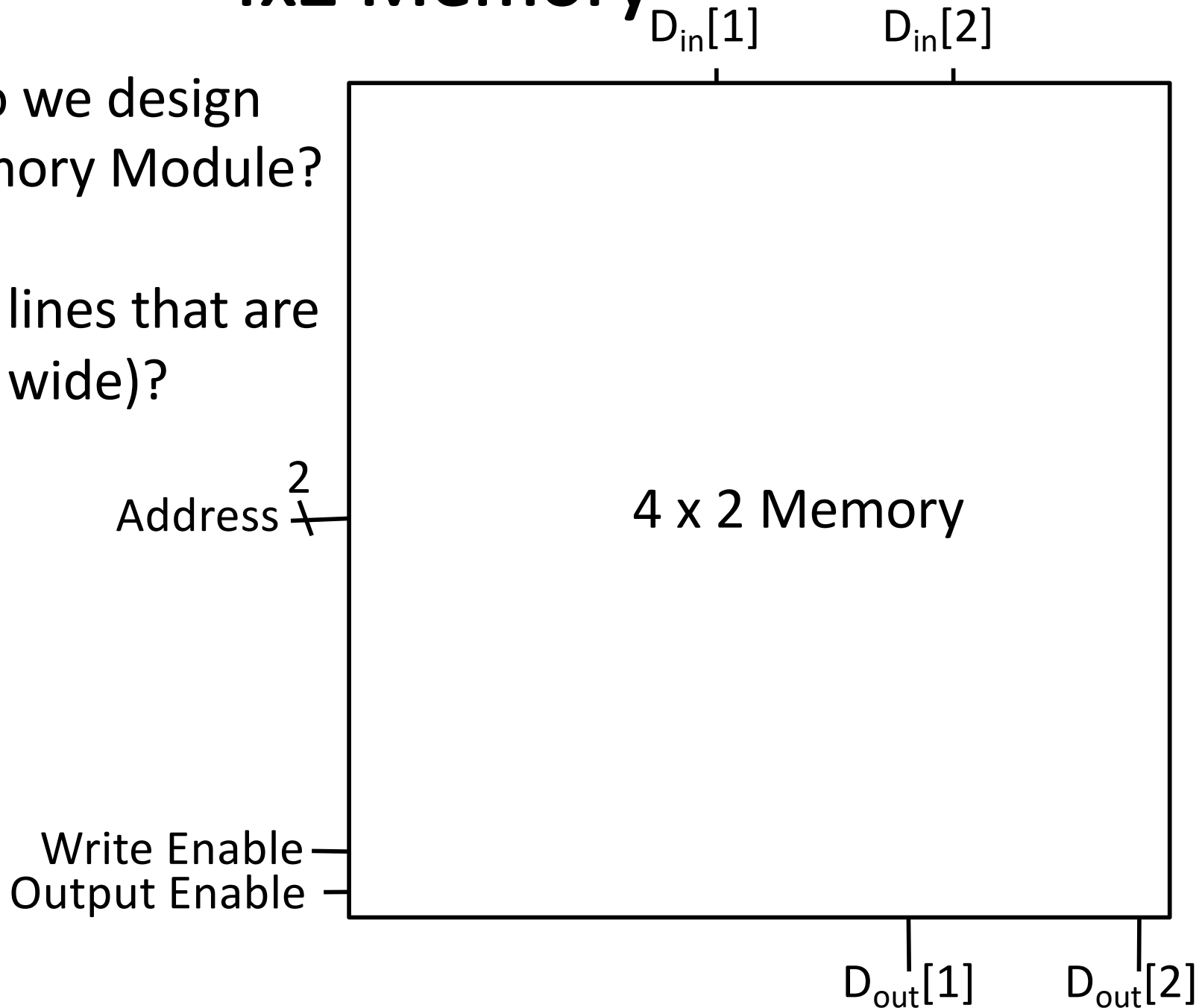
(i.e. 4 word lines that are
each 2 bits wide)?



Memory

E.g. How do we design a 4 x 2 Memory Module?

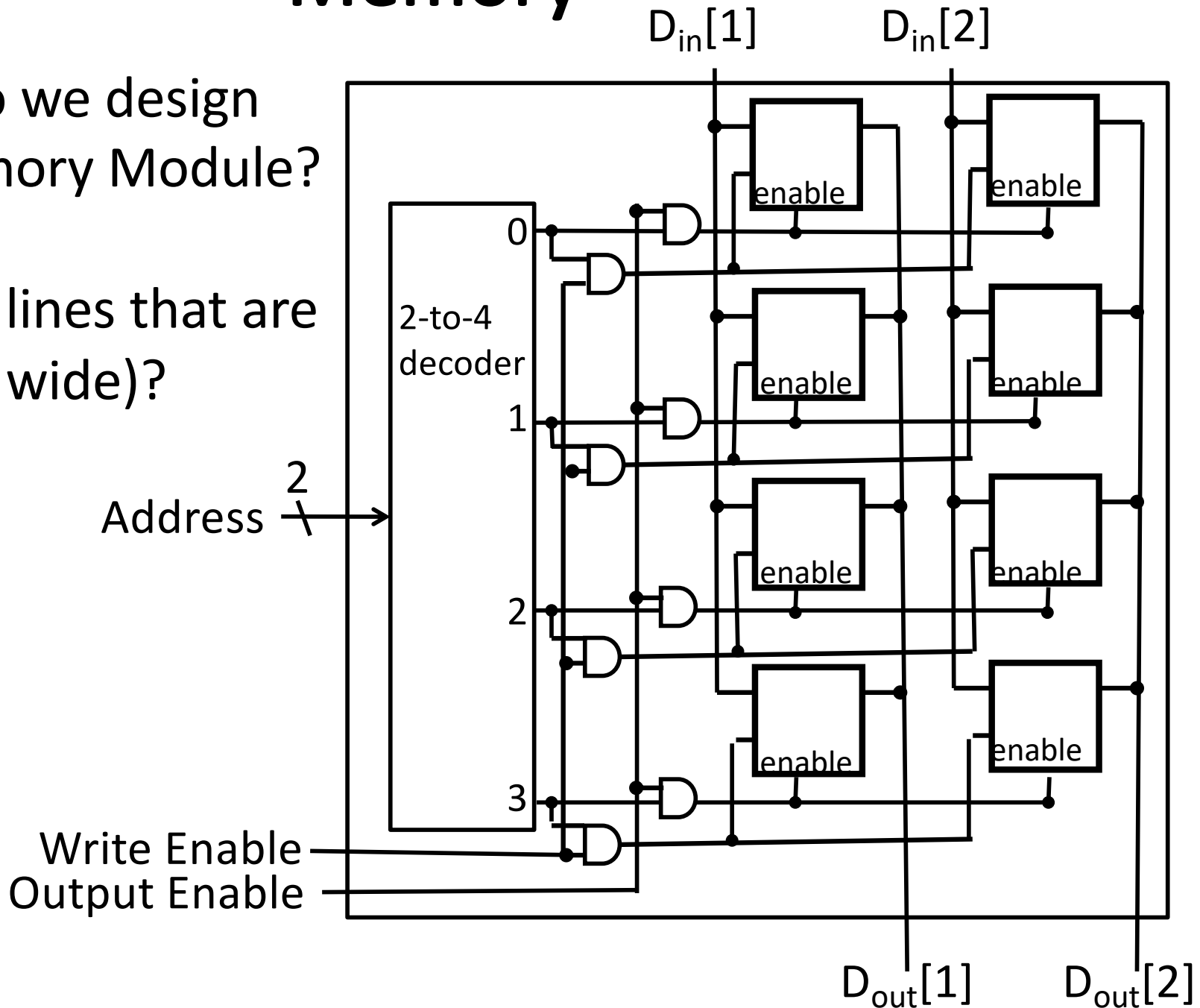(i.e. 4 word lines that are each 2 bits wide)?




Memory

E.g. How do we design a 4 x 2 Memory Module?

(i.e. 4 word lines that are each 2 bits wide)?

Word lines


Write Enable
Output Enable

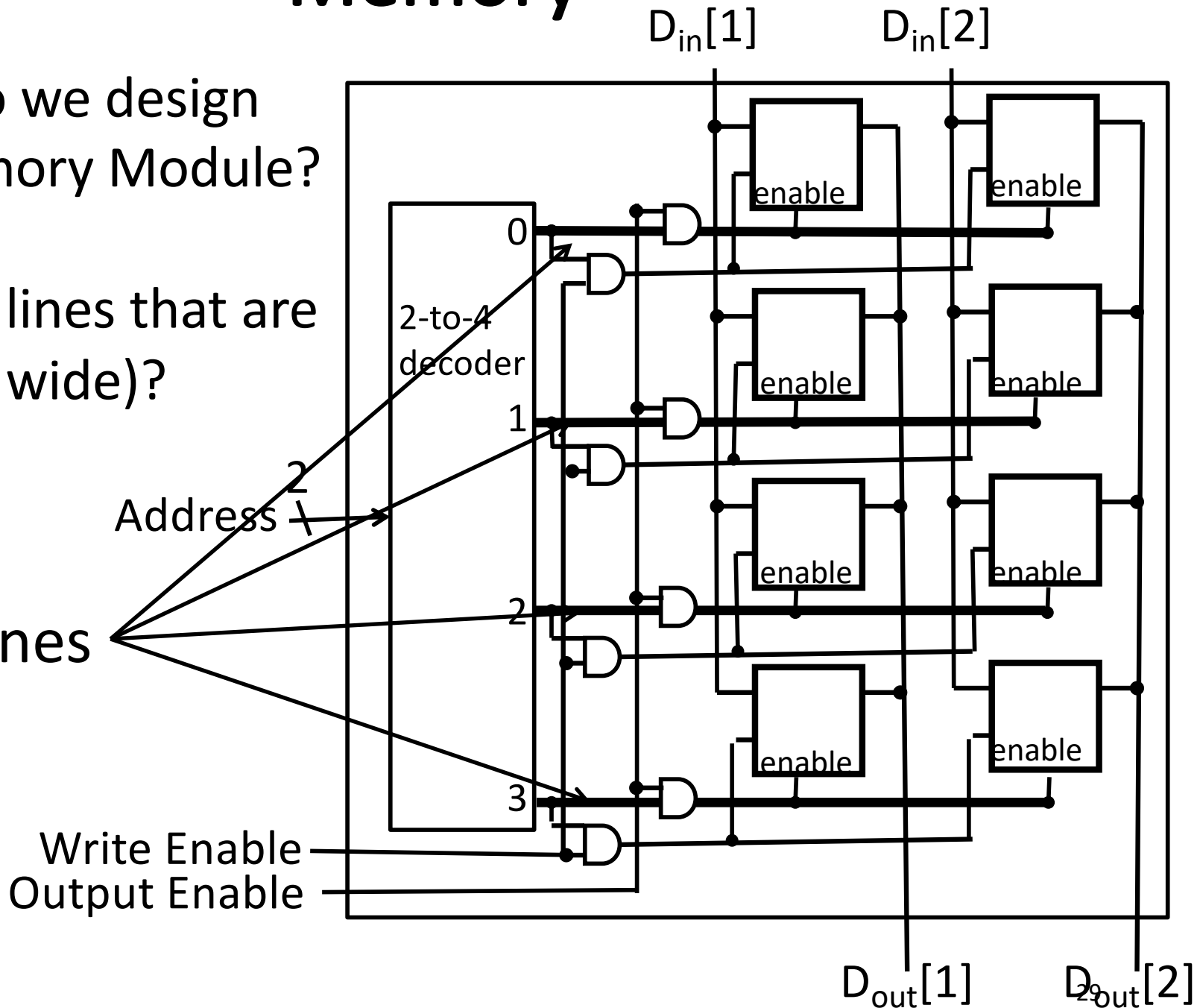



Memory

E.g. How do we design a 4 x 2 Memory Module?

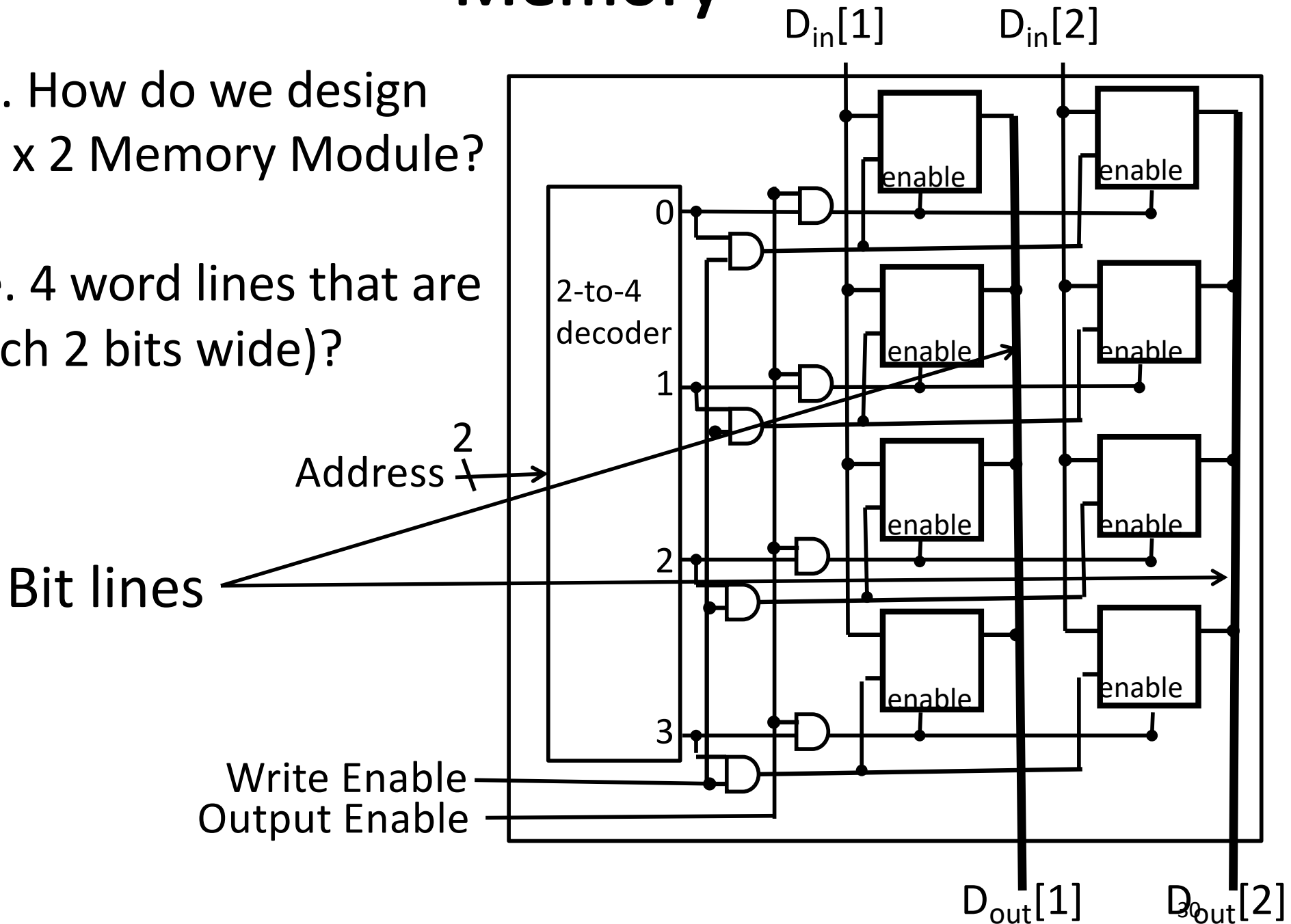(i.e. 4 word lines that are each 2 bits wide)?



MIPS Memory

  

- 32-bit address
- 32-bit data (but byte addressed)
- Enable + 2 bit memory control (mc)
 - 00: read word (4 byte aligned)
 - 01: write byte
 - 10: write halfword (2 byte aligned)
 - 11: write word (4 byte aligned)

In past semesters we have covered the rest of this lecture in the beginning of the Caches Lecture. So if you have no recollection of covering this, it might be because once again we didn't.



SRAM Summary

SRAM


- A few transistors (~ 6) per cell
- Used for working memory (caches)

- But for even higher density...

Dynamic RAM: DRAM

Dynamic-RAM (DRAM)

- Data values require constant refresh

 


Each cell stores one bit, and requires 1 transistors

Dynamic RAM: DRAM

Dynamic-RAM (DRAM)

- Data values require constant refresh

 

Each cell stores one bit, and requires 1 transistors

DRAM vs. SRAM

Single transistor vs. many gates

- Denser, cheaper (\$30/1GB vs. \$30/2MB)
- But more complicated, and has analog sensing

Also needs refresh

- Read and write back...
- ...every few milliseconds
- Organized in 2D grid, so can do rows at a time
- Chip can do refresh internally

Hence... slower and energy inefficient

Memory

Register File tradeoffs

- + Very fast (a few gate delays for both read and write)
- + Adding extra ports is straightforward
- Expensive, doesn't scale
- Volatile

Volatile Memory alternatives: SRAM, DRAM, ...

- Slower
- + Cheaper, and scales well
- Volatile

Non-Volatile Memory (NV-RAM): Flash, EEPROM, ...

- + Scales well
- Limited lifetime; degrades after 100000 to 1M writes