

# State


CS 3410: Computer System Organization and Programming



# Are you happy about the Superbowl

0


Yes, I am Eagles fan!

 


No. I like KC or another team




Don't care

 

 
I was working on A3, Huffman Compression!



# Big Picture: How to Design a Processor

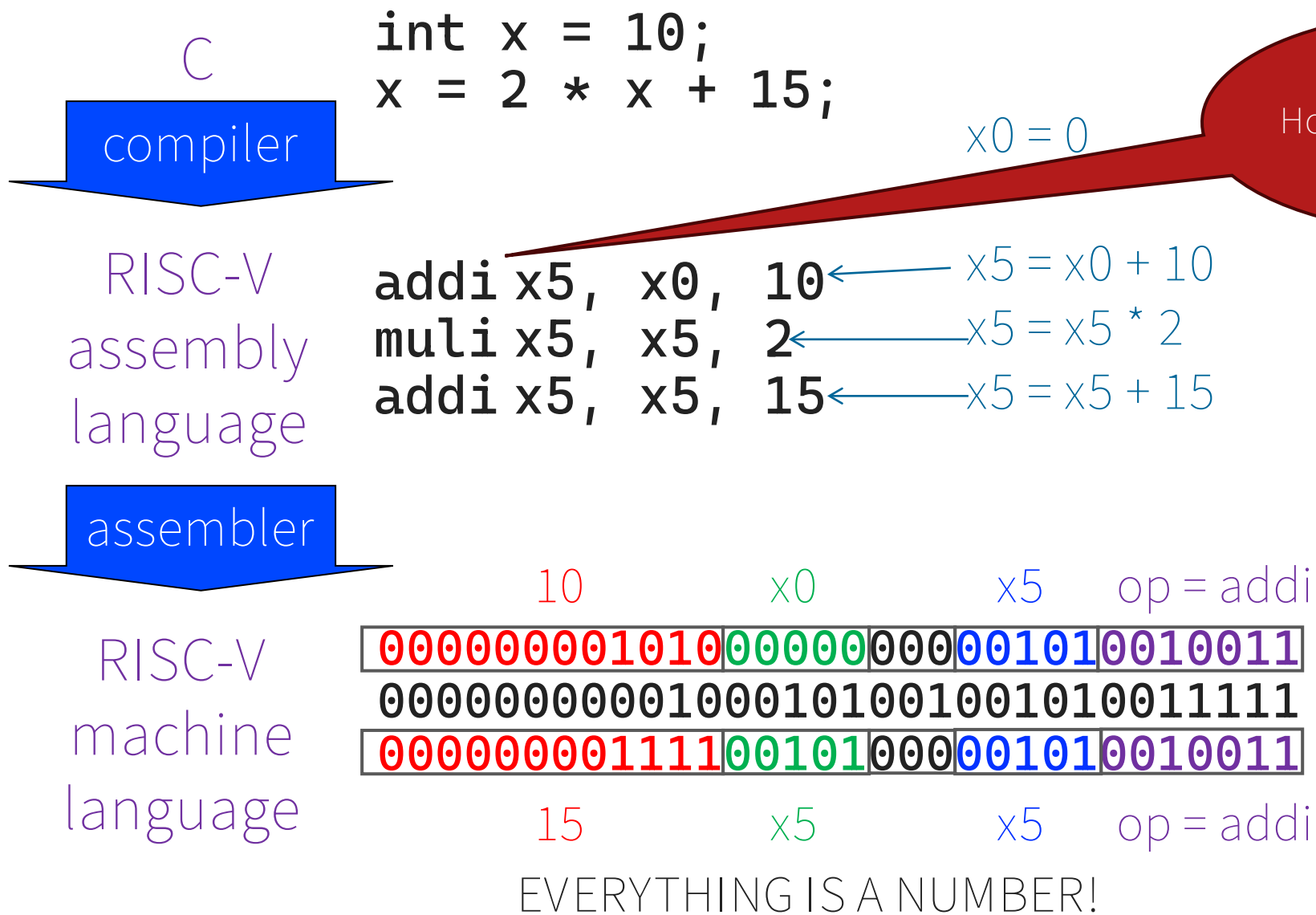


# Big Picture: How to Design a Processor

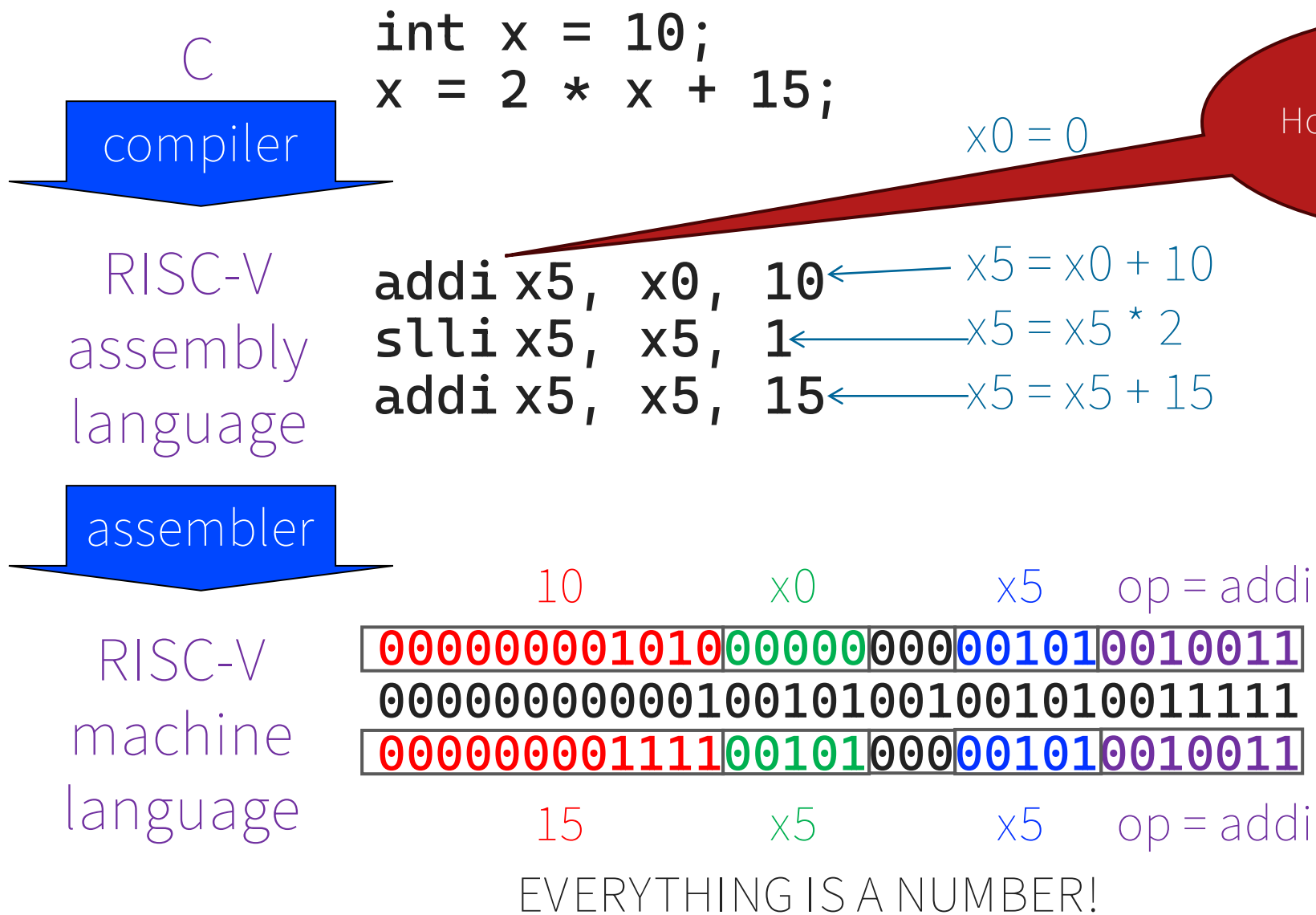

# Big Picture: How to Design a Processor


Processor

 

Runs code; does computations


Doesn't remember anything

Memory

 


Can't compute anything

Stores data

 

# Big Picture: How to Design a Processor


Processor

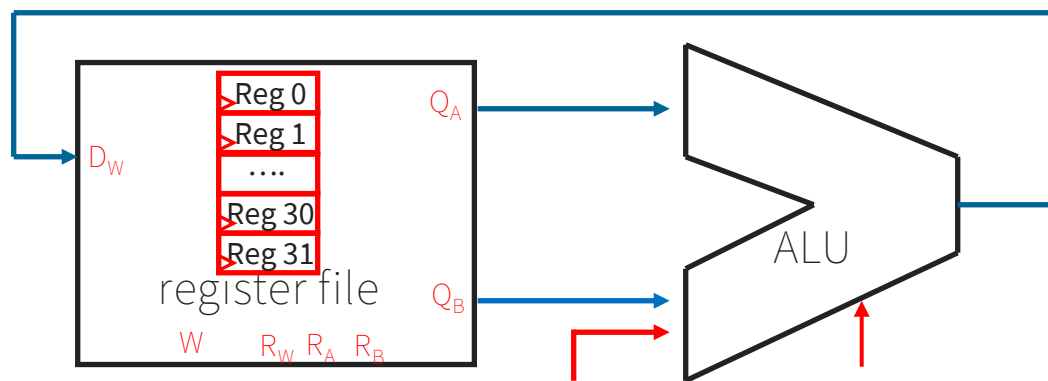

✓ Runs code; does computations


✗ Doesn't remember anything

Memory

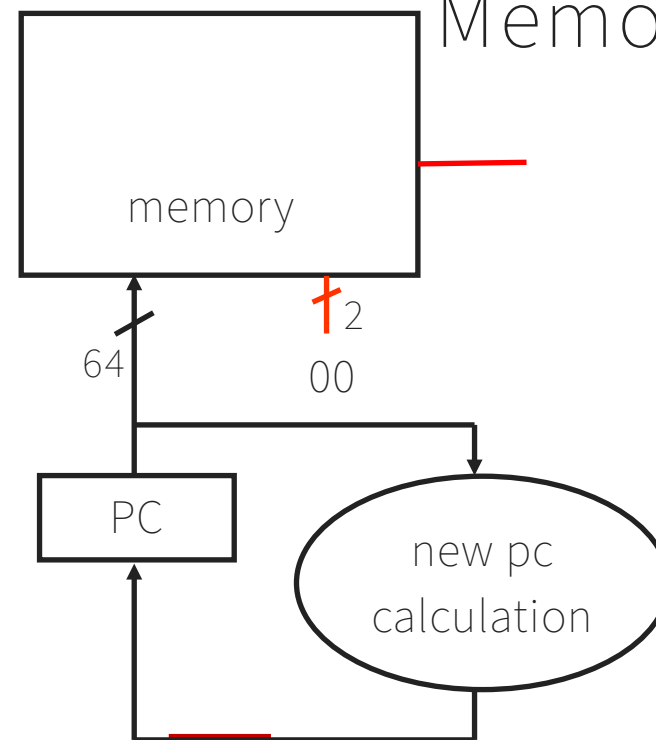


✗ Can't compute anything

✓ Stores data

 


# Big Picture: How to Design a Processor

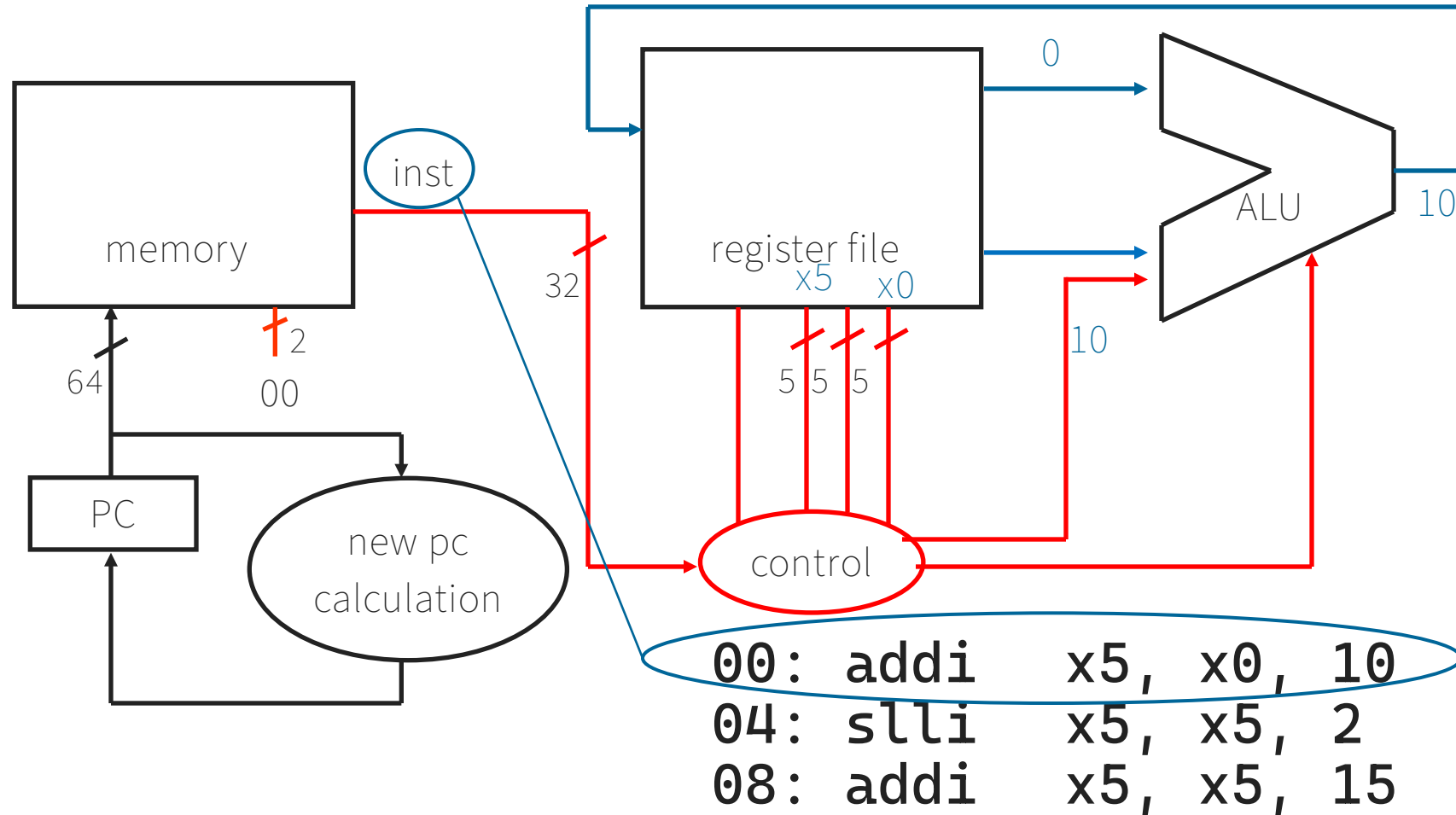
 
# Review


- We can generalize 1-bit Full Adders to 32 bits, 64 bits ...





 
# Review

- We can generalize 1-bit Full Adders to 32 bits, 64 bits ...



 
# Review

- We can generalize 1-bit Full Adders to 32 bits, 64 bits ...



 
# Review

- We can generalize 1-bit Full Adders to 32 bits, 64 bits ...



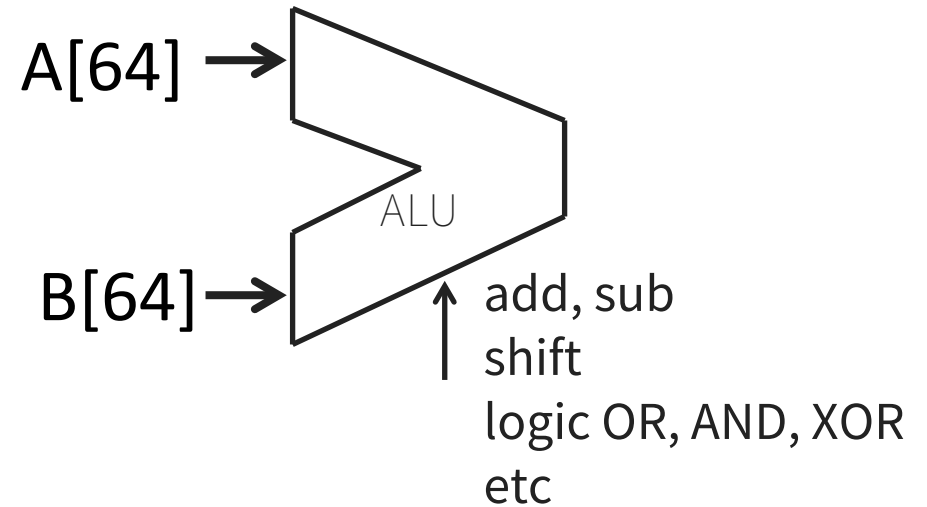
# Review

- We can generalize 1-bit Full Adders to 32 bits, 64 bits ...
- Arithmetic Logic Unit (ALU) adds, subtracts, shifts, logic OR, AND, XOR, etc




# Goal for today

- How do we store results

 
 
# Stateful Components

- Until now is combinational logic
  - Output is computed when inputs are present
  - System has no internal state
  - Nothing computed in the present can depend on what happened in the past!



- Need a way
  - to record data
  - to build stateful circuits
  - state-holding device

# Stateful Components

- Until now is combinational logic
  - Output is computed when inputs are present
  - System has no internal state
  - Nothing computed in the present can depend on what happened in the past!



- Need a way
  - to record data
  - to build stateful circuits
  - state-holding device

# Goals for Today

## State


- How do we store one bit?
  - Attempts at storing (and changing) one bit
    - Set-Reset Latch
    - D Latch
    - D Flip-Flops
- How do we store N bits?
  - Register: storing more than one bit, N-bits



# Goal

How do we store store one bit?


# First Attempt: Unstable Devices

 

# First Attempt: Unstable Devices


Does not work!

- Unstable
- Oscillates wildly!

 



# Second Attempt: Bistable Devices

- Stable and unstable equilibria?

 

A Simple Device


In stable state,  $A \neq B$

  


How do we change the state?



# Third Attempt: Set-Reset Latch

 

# Third Attempt: Set-Reset Latch

 


A	B	OR	NOR
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

S	R	Q	$\bar{Q}$
0	0		
0	1		
1	0		
1	1		

**Set-Reset (S-R) Latch**

Stores a value Q and its complement

# Third Attempt: Set-Reset Latch

 


A	B	OR	NOR
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

S	R	Q	$\bar{Q}$
0	0		
0	1	0	1
1	0		
1	1		

## Set-Reset (S-R) Latch

Stores a value Q and its complement

# Third Attempt: Set-Reset Latch

 

A	B	OR	NOR
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

S	R	Q	$\bar{Q}$
0	0		
0	1	0	1
1	0	?	?
1	1		

## Set-Reset (S-R) Latch

Stores a value Q and its complement

What are the values for Q and  $\bar{Q}$ ?

- a) 0 and 0
- b) 0 and 1
- c) 1 and 0
- d) 1 and 1

PolEV Question



## What are the values for Q and !Q?

0

0 and 0

0%

0 and 1

0%


1 and 0

0%

1 and 1

0%

# Third Attempt: Set-Reset Latch

 

A	B	OR	NOR
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

S	R	Q	$\bar{Q}$
0	0		
0	1	0	1
1	0	1	0
1	1		

## Set-Reset (S-R) Latch


Stores a value  $Q$  and its complement

What are the values for  $Q$  and  $\bar{Q}$ ?

- a) 0 and 0
- b) 0 and 1
- c) 1 and 0
- d) 1 and 1

PolEV Question

# Third Attempt: Set-Reset Latch

 


A	B	OR	NOR
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

S	R	Q	$\bar{Q}$
0	0	Q	$\bar{Q}$
0	1	0	1
1	0	1	0
1	1		

Set-Reset (S-R) Latch  
Stores a value Q and its complement

# Third Attempt: Set-Reset Latch

 

A	B	OR	NOR
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

1

S	R	Q	Q̄
0	0	Q	Q̄
0	1	0	1
1	0	1	0
1	1	?	?

Set-Reset (S-R) Latch

Stores a value Q and its complement

What happens when S,R changes from 1,1 to 0,0?

# What's wrong with the SR Latch? **PolIEV Question**

- A. Q is undefined when  $S=1$  and  $R=1$   
(That's why this is called the forbidden state.)
- B. Q oscillates between 0 and 1 when the inputs transition from 1,1  
→ 0,0
- C. The SR Latch is problematic b/c it has two outputs to store a single bit.
- D. There is nothing wrong with the SR Latch!



## What's wrong with the SR Latch?

0

Q is undefined when  $S=1$  and  $R=1$  (That's why this is called the forbidden state.)

0%

Q oscillates between 0 and 1 when the inputs transition from  $1,1 \rightarrow 0,0$

0%


The SR Latch is problematic b/c it has two outputs to store a single bit.

0%

There is nothing wrong with the SR Latch!

0%

# Third Attempt: Set-Reset Latch

 

A	B	OR	NOR
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

S	R	Q	$\bar{Q}$
0	0	Q	$\bar{Q}$
0	1	0	1
1	0	1	0
1	1	forbidden	



## Set-Reset (S-R) Latch

Stores a value Q and its complement

What happens when S,R changes from 1,1 to 0,0?

Q and  $\bar{Q}$  become unstable and will oscillate wildly between values 0,0 to 1,1 to 0,0 to 1,1 ...

# Third Attempt: Set-Reset Latch

  

S	R	Q	$\bar{Q}$	
0	0	Q	$\bar{Q}$	hold
0	1	0	1	reset
1	0	1	0	set
1	1	forbidden		

## Set-Reset (S-R) Latch

Stores a value Q and its complement



# Takeaway



Set-Reset (SR) Latch can store one bit and we can change the value of the stored bit. But, SR Latch has a forbidden state.



# Next Goal

How do we avoid the forbidden state of S-R Latch?

# Fourth Attempt: (Unclocked) D Latch

  



Fill in the truth table?

D	Q	$\bar{Q}$
0		
1		

A	B	OR	NOR
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0



# Fourth Attempt: (Unclocked) D Latch

  

Fill in the truth table?

D	Q	$\bar{Q}$
0	0	1
1	1	0

Data (D) Latch

- Easier to use than an SR latch
- No possibility of entering an undefined state

When D changes, Q changes

- ... immediately (...after a delay of 2 Ors and 2 NOTs)

A	B	OR	NOR
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

Need to control when the output changes

# Takeaway

Set-Reset (SR) Latch can store one bit and we can change the value of the stored bit. But, SR Latch has a forbidden state.

(Unclocked) D Latch can store and change a bit like an SR Latch while avoiding the forbidden state.


# Next Goal

How do we coordinate state changes to a D Latch?
 
# Aside: Clocks

Clock helps coordinate state changes

- Usually generated by an oscillating crystal
- Fixed period
- Frequency =  $1/\text{period}$



# Clock Disciplines

## Level sensitive


- State changes when clock is high (or low)




## Edge triggered

- State changes at clock edge

**positive edge-triggered**

 

**negative edge-triggered**

 




# Clock Methodology

## Clock Methodology

- Negative edge, synchronous

 


Edge-Triggered → signals must be stable near falling edge


“near” = before and after

$t_{\text{setup}}$        $t_{\text{hold}}$

# Round 2: D Latch (1)

 


 - Inverter prevents SR Latch from entering 1,1 state




	D	Q	$\bar{Q}$	
	0			<i>Reset</i>
	1			<i>Set</i>

# Round 2: D Latch (1)

 

 
- Inverter prevents SR Latch from entering 1,1 state



	D	Q	$\bar{Q}$	
	0	0	1	<i>Reset</i>
	1	1	0	<i>Set</i>



# Round 2: D Latch (1)

 


- Level sensitive
- Inverter prevents SR Latch from entering 1,1 state
- C enables changes


C = 1, D Latch *transparent*:  
set/reset (according to D)

C = 0, D Latch *opaque*:  
keep state (ignore D)

C	D	Q	$\bar{Q}$	
0	0			No Change
0	1			
1	0			Reset
1	1			Set

 

# Round 2: D Latch (1)

 


- Level sensitive
- Inverter prevents SR Latch from entering 1,1 state
- C enables changes

C = 1, D Latch *transparent*:  
set/reset (according to D)


C = 0, D Latch *opaque*:  
keep state (ignore D)

S	R	Q	$\bar{Q}$	
0	0	Q	$\bar{Q}$	hold
0	1	0	1	reset
1	0	1	0	set
1	1	forbidden		

 


C	D	Q	$\bar{Q}$	
0	0	Q	$\bar{Q}$	No Change
0	1	Q	$\bar{Q}$	
1	0	0	1	Reset
1	1	1	0	Set

# PolIEV Question

 

What is the value of Q at A & B?

 - a)  $A = 0, B = 0$
- b)  $A = 0, B = 1$
- c)  $A = 1, B = 0$
- d)  $A = 1, B = 1$



clk	D	Q	$\bar{Q}$
0	0	Q	$\bar{Q}$
0	1	Q	$\bar{Q}$
1	0	0	1
1	1	1	0

## What is the value of Q at A & B?

0

A = 0, B = 0

0%

A = 0, B = 1

0%


A = 1, B = 0

0%

A = 1, B = 1


0%

# PolIEV Question

 

What is the value of Q at A & B?

 
- a)  $A = 0, B = 0$
- b)  $A = 0, B = 1$
- c)  $A = 1, B = 0$
- d)  $A = 1, B = 1$



clk	D	Q	$\bar{Q}$
0	0	Q	$\bar{Q}$
0	1	Q	$\bar{Q}$
1	0	0	1
1	1	1	0



# PolIEV Question

 


## Level Sensitive D Latch

Clock high:

set/reset (according to D)


Clock low:

keep state (ignore D)

 

clk	D	Q	$\bar{Q}$
0	0	Q	$\bar{Q}$
0	1	Q	$\bar{Q}$
1	0	0	1
1	1	1	0

# Round 3: D Flip-Flop

 

- Edge-Triggered
- Data captured when clock high
- Output changes only on falling edges




# Round 3: D Flip-Flop

Clock = 1: L1 transparent

L2 opaque

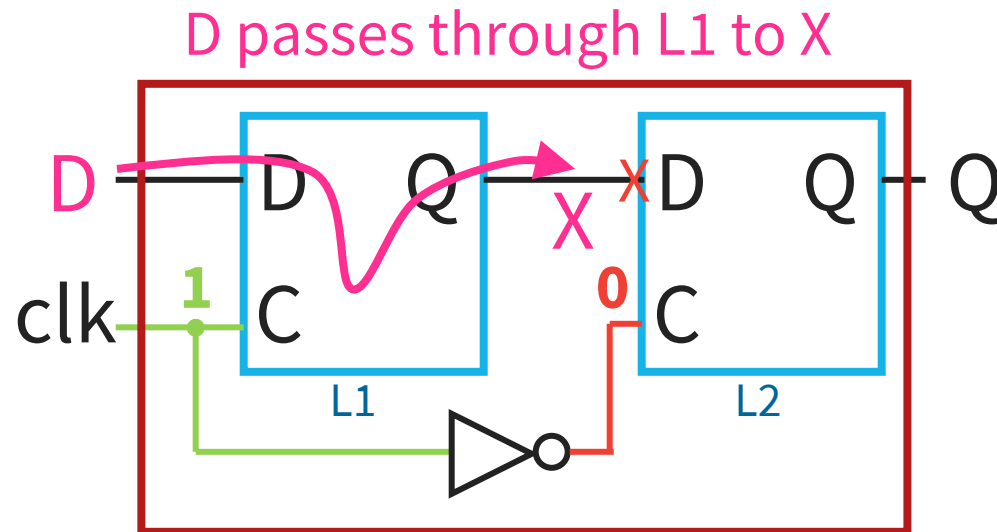
When CLK rises (0 → 1),  
now X can change,  
Q does not change




Clock = 0: L1 opaque

L2 transparent

 When **CLK falls** (1 → 0),  
Q gets X, X cannot change




# PolIEV Question – start here

 

What is the value of Q at A & B?

 - a)  $A = 0, B = 0$
- b)  $A = 0, B = 1$
- c)  $A = 1, B = 0$
- d)  $A = 1, B = 1$



## What is the value of Q at A & B? (take two)

0

A = 0, B = 0

0%

A = 0, B = 1

0%


A = 1, B = 0

0%

A = 1, B = 1


0%

# PolIEV Question – start here

 


What is the value of Q at A & B?

 - a)  $A = 0, B = 0$
- b)  $A = 0, B = 1$
- c)  $A = 1, B = 0$**
- d)  $A = 1, B = 1$




# Edge-Triggered D Flip-Flop

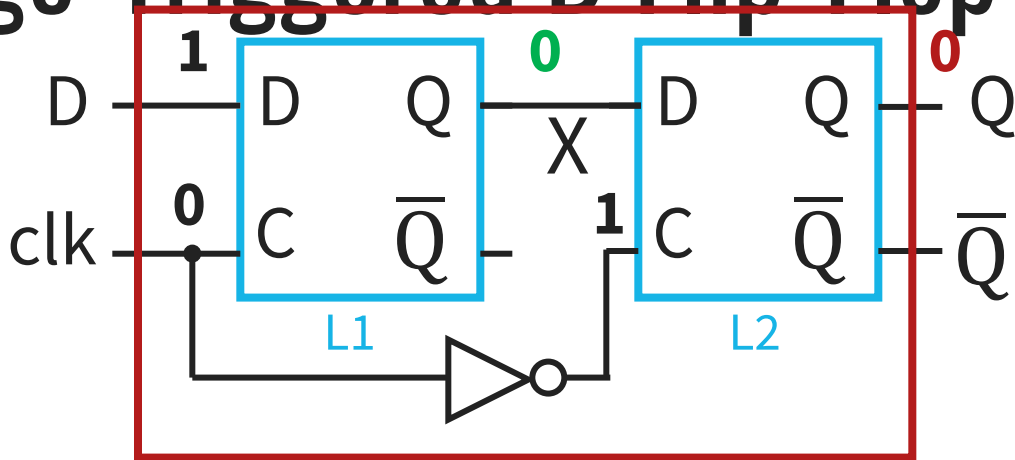

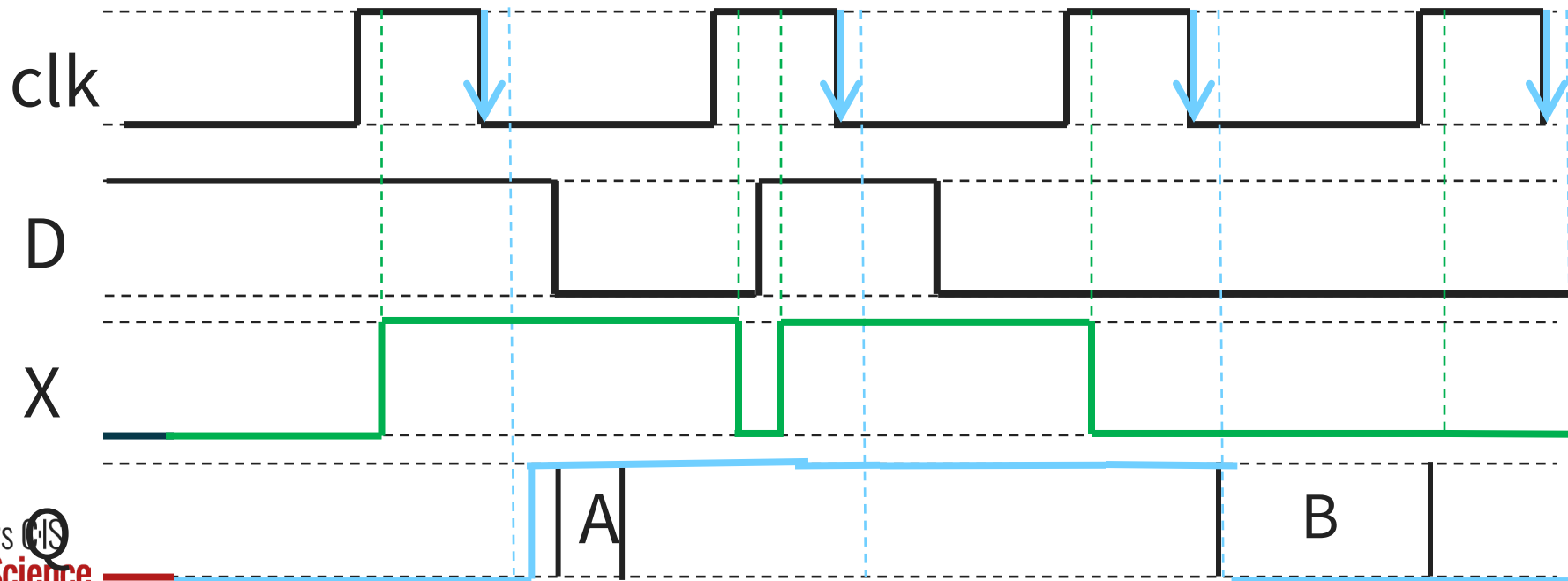
## D Flip-Flop

- Edge-Triggered
- Data captured when clock is high
- Output changes only on falling edges




# Building a D Flip Flop (DFF)

 


Step 1: Create an SR Latch

Set	Reset	Q
0	0	Q
0	1	0
1	0	1
1	1	?

 




# Building a D Flip Flop (DFF)

 


Step 1: Create an SR Latch

Step 2: Create a D Latch

Clk	Data	Q
0	0	Q
0	1	Q
1	0	0
1	1	1

 


# Building a D Flip Flop (DFF)

 

Step 1: Create an SR Latch

Step 2: Create a D Latch

 Step 3: Duplicate the D Latch, chain together



# Takeaway



Set-Reset (SR) Latch can store one bit and we can change the value of the stored bit. But, SR Latch has a forbidden state.



(Unlocked) D Latch can store and change a bit like an SR Latch while avoiding a forbidden state.




An Edge-Triggered D Flip-Flop (aka Master-Slave D Flip-Flop) stores one bit. The bit can be changed in a synchronized fashion on the edge of a clock signal.

# Next Goal

How do we store more than one bit,  $N$  bits?




# Registers

 

## Register


- D flip-flops in parallel

# Registers

 

 
## Register

- D flip-flops in parallel
- shared clock
- extra clocked inputs: write\_enable, reset, ...




# Registers

 
 
## Register

- D flip-flops in parallel
- shared clock
- extra clocked inputs: write\_enable, reset, ...



# Takeaway

Set-Reset (SR) Latch can store one bit and we can change the value of the stored bit. But, SR Latch has a forbidden state.


(Unclocked) D Latch can store and change a bit like an SR Latch while avoiding a forbidden state.

An Edge-Triggered D Flip-Flop (aka Master-Slave D Flip-Flop) stores one bit. The bit can be changed in a synchronized fashion on the edge of a clock signal.

An  $N$ -bit register stores  $N$ -bits. It is created with  $N$  D-Flip-Flops in parallel along with a shared clock.




# Registers

 

 
## Register

- D flip-flops in parallel
- shared clock
- extra clocked inputs: write\_enable, reset, ...




# Big Picture: How to Design a Processor

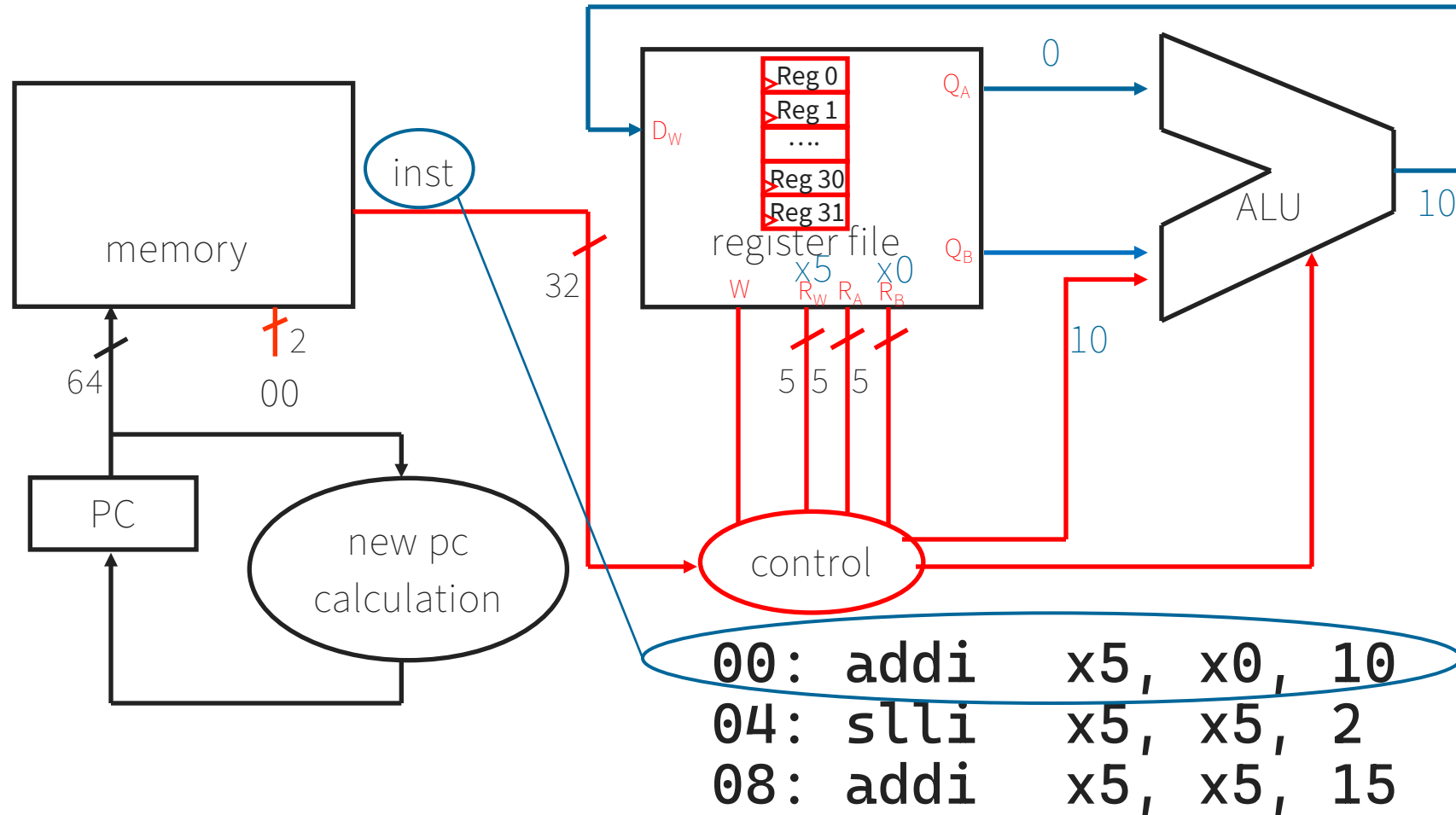

# Big Picture: How to Design a Processor
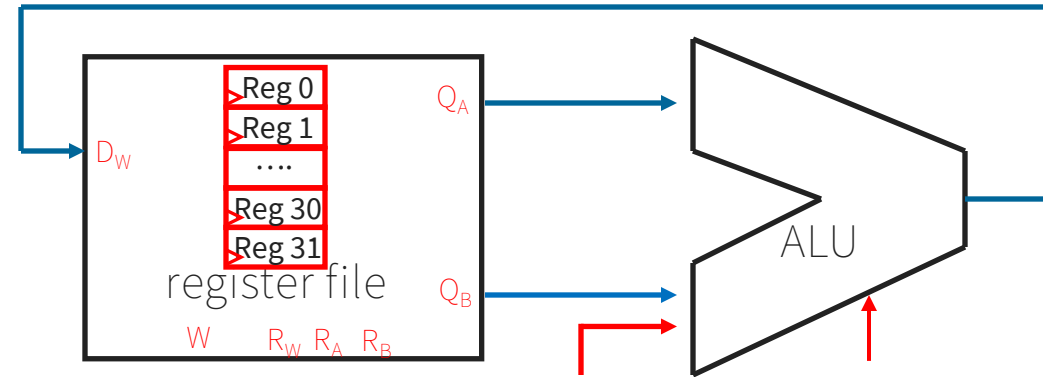
## Register File

- N read/write registers
- Indexed by register number




## Registers

- Numbered from 0 to 31
- Can be referred by number:  $x0, x1, x2, \dots, x31$ 
  - May also see  $\$0, \$1, \$2$  or  $r0, r1, r2$
- Convention, each register also has a name:
  - $x16 - x23 \rightarrow s0 - s7$  ("s registers")
  - $x8 - x15 \rightarrow t0 - t7$  ("t registers")

```
00: addi    x5, x0, 10
04: slli    x5, x5, 2
08: addi    x5, x5, 15
```



# Big Picture: How to Design a Processor

 


PC is register!

- PC is the Program Counter
- Stores the memory address of the next instruction

```
00: addi    x5, x0, 10
04: slli    x5, x5, 2
08: addi    x5, x5, 15
```



# Big Picture: How to Design a Processor

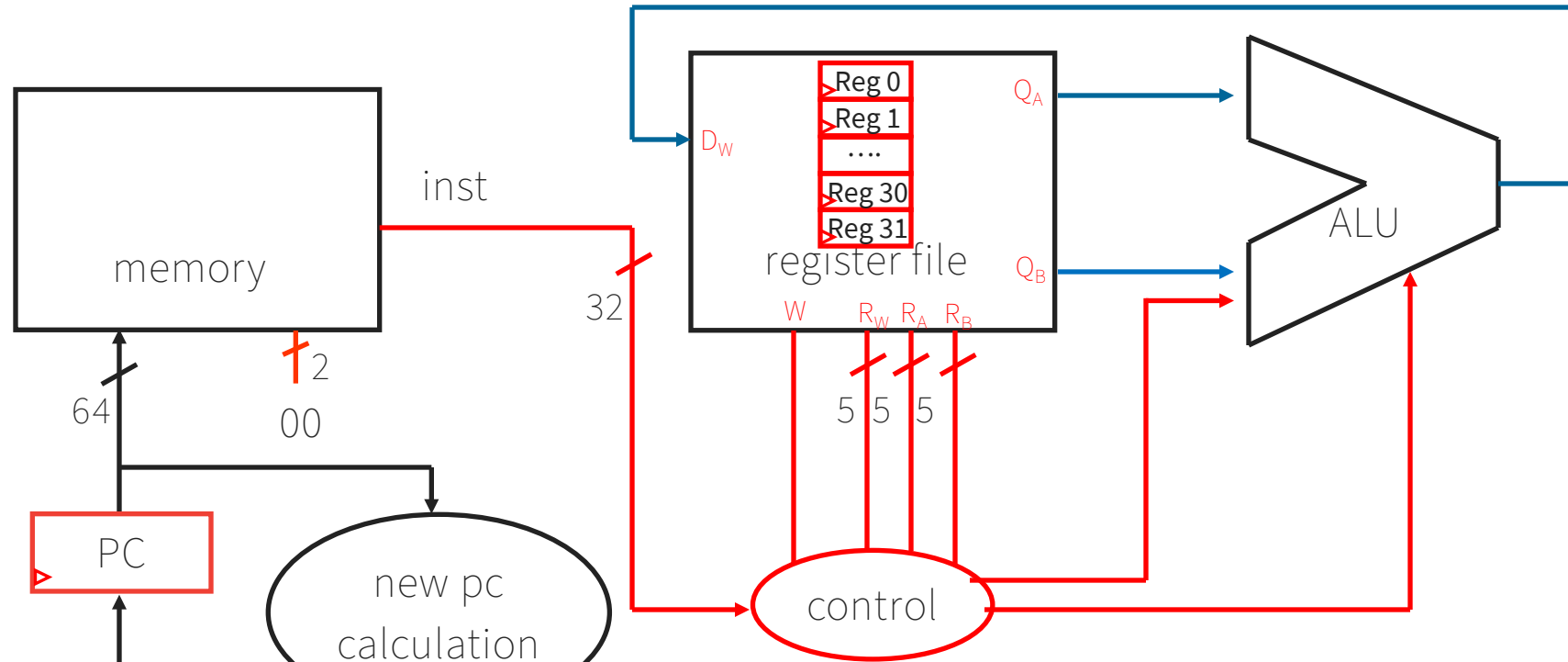

```

00: addi    x5, x0, 10
04: slli   x5, x5, 2
08: addi   x5, x5, 15
    
```



# Takeaway

Set-Reset (SR) Latch can store one bit and we can change the value of the stored bit. But, SR Latch has a forbidden state.

(Unclocked) D Latch can store and change a bit like an SR Latch while avoiding a forbidden state.

An Edge-Triggered D Flip-Flop (aka Master-Slave D Flip-Flop) stores one bit. The bit can be changed in a synchronized fashion on the edge of a clock signal.

An  $N$ -bit register stores  $N$ -bits. It is created with  $N$  D-Flip-Flops in parallel along with a shared clock.

# Summary

We store data values

- Stateful circuit elements (D Flip Flops, Registers, ...)
- Clock to synchronize state changes