

State

CS 3410: Computer System Organization and Programming



Big Picture: How to Design a Processor

C

```
int x = 10;  
x = 2 * x + 15;
```

compiler

RISC-V
assembly
language

```
addi x5, x0, 10 ← x5 = x0 + 10  
mul  x5, x5, 2  ← x5 = x5 * 2  
addi x5, x5, 15 ← x5 = x5 + 15
```

x0 = 0

How does add work?

assembler

RISC-V
machine
language

```
10      x0      x5      op = addi  
0000000010100000000001010010011  
00000000001000101001001010011111  
15      x5      x5      op = addi  
00000000111100101000001010011
```

EVERYTHING IS A NUMBER!

Big Picture: How to Design a Processor

C

```
int x = 10;  
x = 2 * x + 15;
```

compiler

RISC-V
assembly
language

```
addi x5, x0, 10 ← x5 = x0 + 10  
slli x5, x5, 1 ← x5 = x5 * 2  
addi x5, x5, 15 ← x5 = x5 + 15
```

x0 = 0

How does add work?

assembler


RISC-V
machine
language

```
10      x0      x5      op = addi  
0000000010100000000001010010011  
00000000000010010100100101001111  
000000001111001010000001010010011  
15      x5      x5      op = addi
```

EVERYTHING IS A NUMBER!

Big Picture: How to Design a Processor

Processor

 


Runs code; does computations



Doesn't remember anything


Memory

 


Can't compute anything




Stores data

 

Big Picture: How to Design a Processor

 


Processor

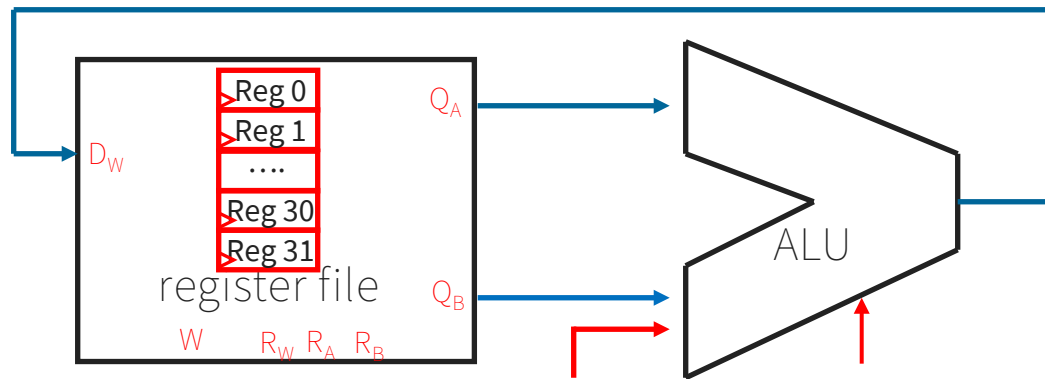

✓ Runs code; does computations

✗ Doesn't remember anything


Memory

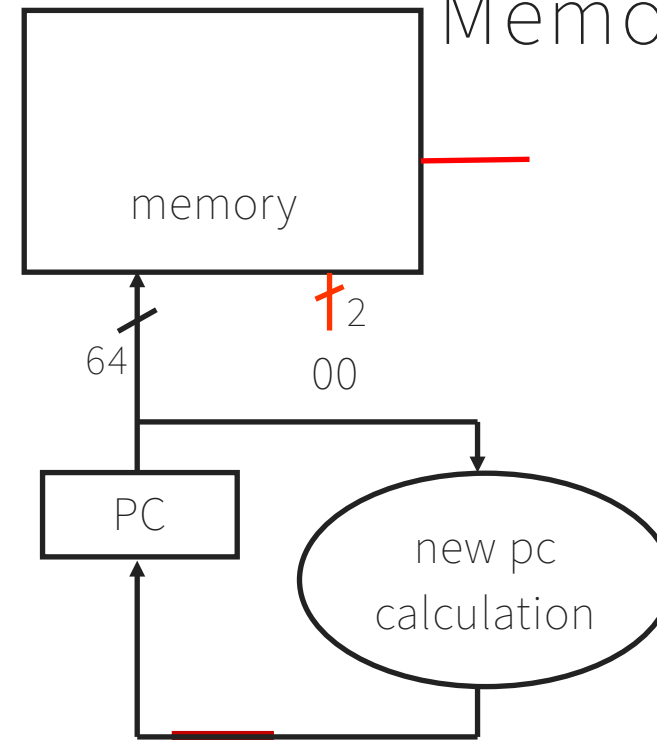

✗ Can't compute anything


✓ Stores data

Big Picture: How to Design a Processor

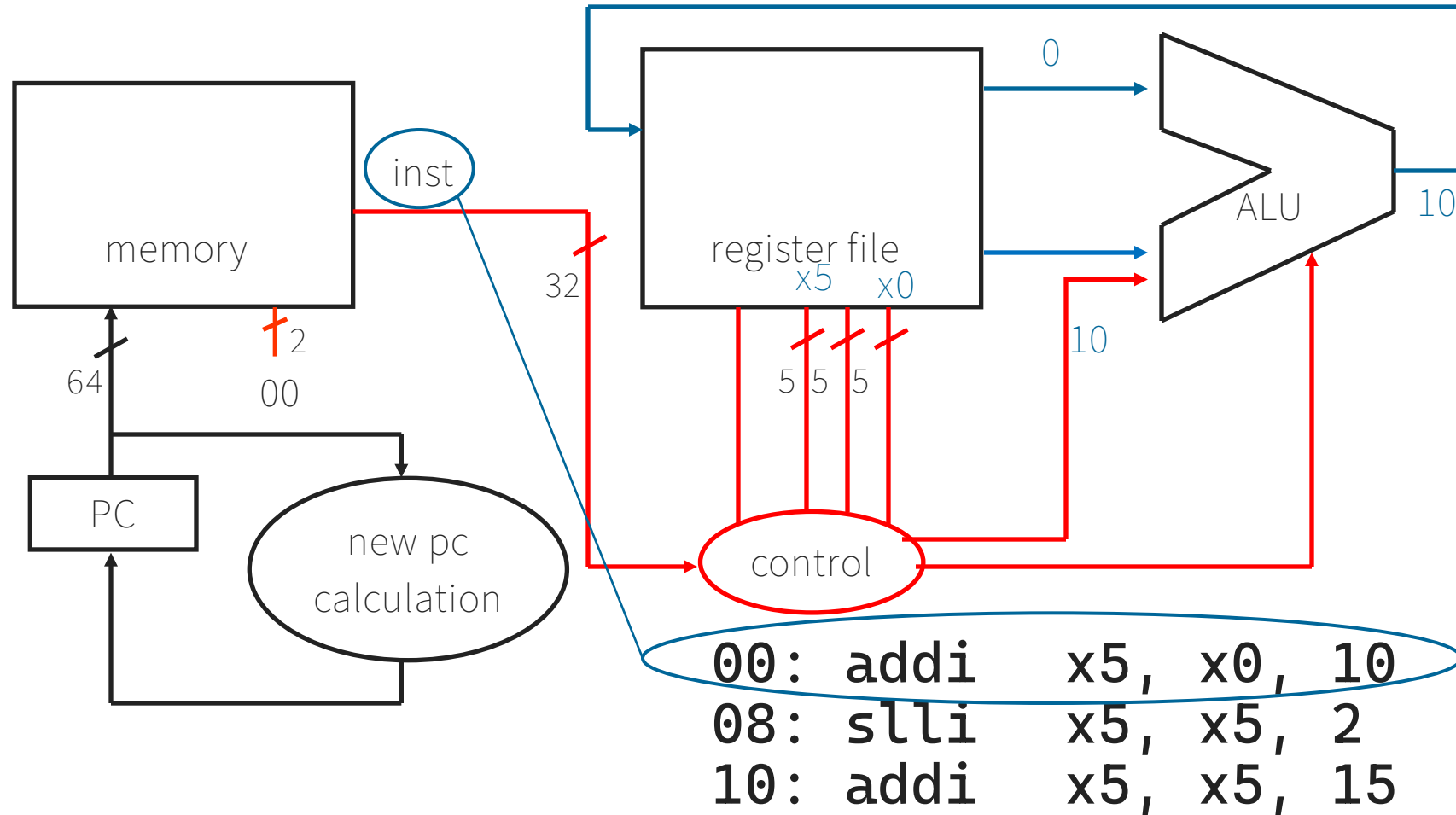


Review

 - We can generalize 1-bit Full Adders to 32 bits, 64 bits ...




Review

 - We can generalize 1-bit Full Adders to 32 bits, 64 bits ...




Review

 - We can generalize 1-bit Full Adders to 32 bits, 64 bits ...




Review

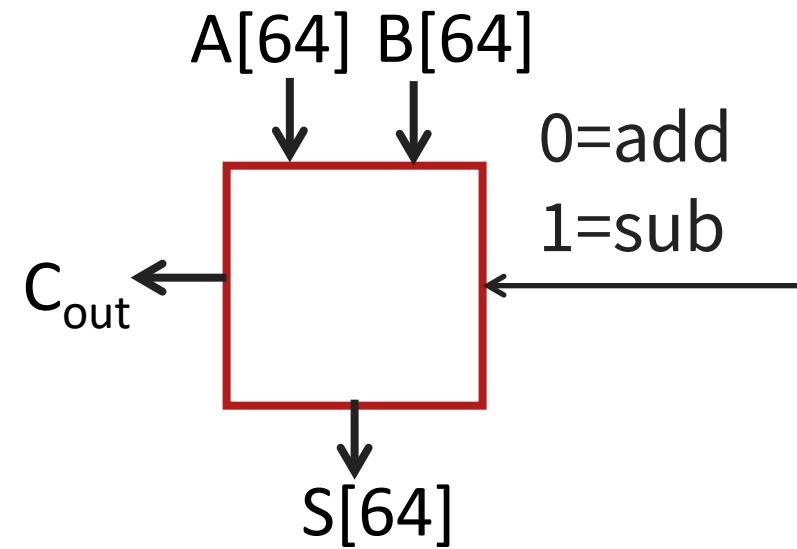- We can generalize 1-bit Full Adders to 32 bits, 64 bits ...




Review

 - We can generalize 1-bit Full Adders to 32 bits, 64 bits ...
- Arithmetic Logic Unit (ALU) adds, subtracts, shifts, logic OR, AND, XOR, etc




Goal for today

- How do we store results

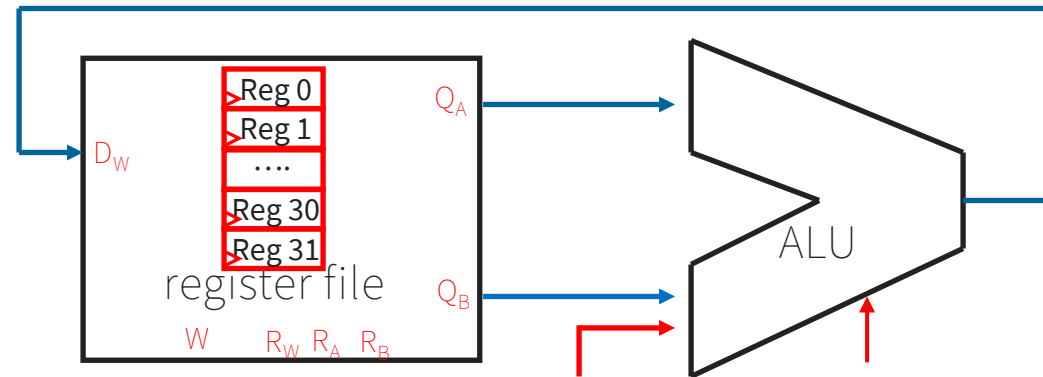

Stateful Components

 - Until now is combinational logic
 - Output is computed when inputs are present
 - System has no internal state
 - Nothing computed in the present can depend on what happened in the past!



- Need a way
 - to record data
 - to build stateful circuits
 - state-holding device

Stateful Components

- Until now is combinational logic
 - Output is computed when inputs are present
 - System has no internal state
 - Nothing computed in the present can depend on what happened in the past!



- Need a way
 - to record data
 - to build stateful circuits
 - state-holding device

Goals for Today


State

- How do we store one bit?
- Attempts at storing (and changing) one bit
 - Set-Reset Latch
 - D Latch
 - D Flip-Flops
- How do we store N bits?
 - Register: storing more than one bit, N-bits

Goal


How do we store store one bit?

First Attempt: Unstable Devices

 



Second Attempt: Bistable Devices

- Stable and unstable equilibria?

 


A Simple Device


In stable state, $A \neq B$

  

Third Attempt: Set-Reset Latch

 

Third Attempt: Set-Reset Latch

 



A	B	OR	NOR
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

S	R	Q	\bar{Q}
0	0		
0	1		
1	0		
1	1		

Set-Reset (S-R) Latch

Stores a value Q and its complement

Third Attempt: Set-Reset Latch

  

S	R	Q	\bar{Q}	
0	0	Q	\bar{Q}	hold
0	1	0	1	reset
1	0	1	0	set
1	1	forbidden		

Set-Reset (S-R) Latch

Stores a value Q and its complement

Takeaway



Set-Reset (SR) Latch can store one bit and we can change the value of the stored bit. But, SR Latch has a forbidden state.

Next Goal

How do we avoid the forbidden state of S-R Latch?



Fourth Attempt: (Unclocked) D Latch

 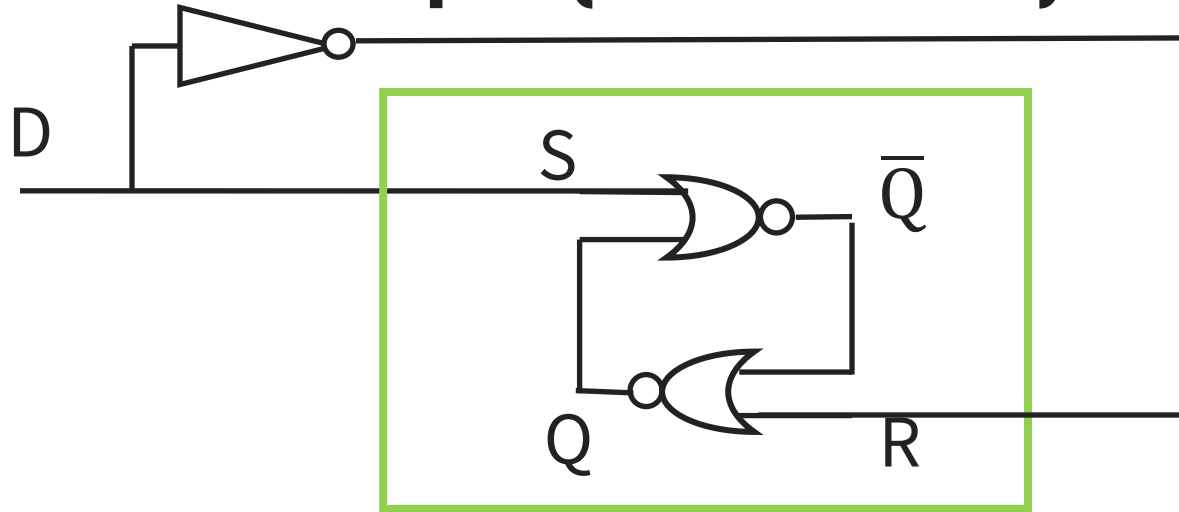

Fill in the truth table?

D	Q	\bar{Q}
0		
1		

A	B	OR	NOR
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

Takeaway

Set-Reset (SR) Latch can store one bit and we can change the value of the stored bit. But, SR Latch has a forbidden state.

(Unclocked) D Latch can store and change a bit like an SR Latch while avoiding the forbidden state.


Next Goal

How do we coordinate state changes to a D Latch?

Aside: Clocks

Clock helps coordinate state changes

 - Usually generated by an oscillating crystal
- Fixed period
- Frequency = $1/\text{period}$



Clock Disciplines

Level sensitive

- State changes when clock is high (or low)




Edge triggered

- State changes at clock edge

positive edge-triggered




negative edge-triggered

 

Clock Methodology

Clock Methodology

- Negative edge, synchronous

 


Edge-Triggered \rightarrow signals must be stable near falling edge


“near” = before and after

t_{setup} t_{hold}

Round 2: D Latch (1)

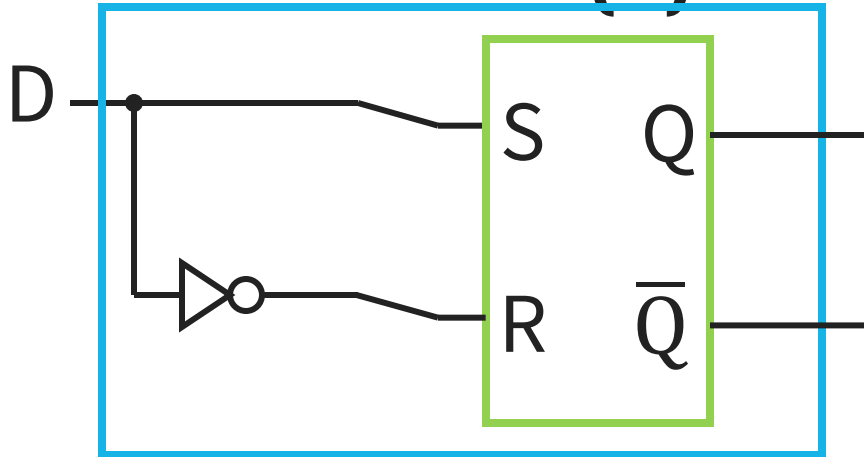


 - Inverter prevents SR Latch from entering 1,1 state




	D	Q	\bar{Q}	
	0			<i>Reset</i>
	1			<i>Set</i>

Round 2: D Latch (1)

 


 - Inverter prevents SR Latch from entering 1,1 state



	D	Q	\bar{Q}	
	0	0	1	<i>Reset</i>
	1	1	0	<i>Set</i>


Round 2: D Latch (1)

 

- Level sensitive
- Inverter prevents SR Latch from entering 1,1 state
- C enables changes


C = 1, D Latch *transparent*:
set/reset (according to D)

 C = 0, D Latch *opaque*:
keep state (ignore D)



C	D	Q	\bar{Q}	
0	0			No Change
0	1			
1	0			Reset
1	1			Set

Round 2: D Latch (1)

 


- Level sensitive
- Inverter prevents SR Latch from entering 1,1 state
- C enables changes

C = 1, D Latch *transparent*:
set/reset (according to D)


C = 0, D Latch *opaque*:
keep state (ignore D)

S	R	Q	\bar{Q}	
0	0	Q	\bar{Q}	hold
0	1	0	1	reset
1	0	1	0	set
1	1	forbidden		

 


C	D	Q	\bar{Q}	
0	0	Q	\bar{Q}	No Change
0	1	Q	\bar{Q}	
1	0	0	1	Reset
1	1	1	0	Set

PolIEV Question

 


What is the value of Q at A & B?

 - a) $A = 0, B = 0$
- b) $A = 0, B = 1$
- c) $A = 1, B = 0$
- d) $A = 1, B = 1$



clk	D	Q	\bar{Q}
0	0	Q	\bar{Q}
0	1	Q	\bar{Q}
1	0	0	1
1	1	1	0

Round 3: D Flip-Flop

 


- Edge-Triggered
- Data captured when clock high
- Output changes only on falling edges

Round 3: D Flip-Flop

Clock = 1: L1 transparent

L2 opaque

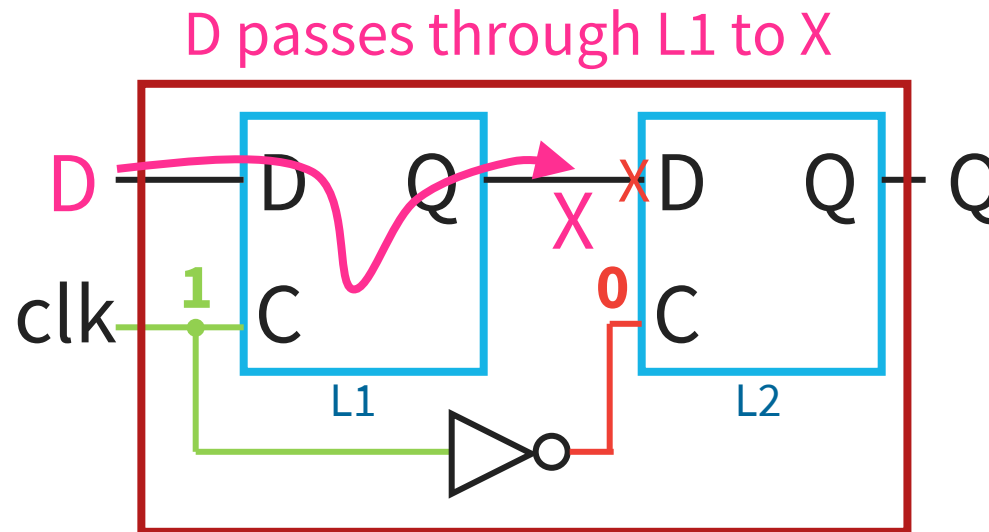When *CLK* rises (0→1),
now *X* can change,
Q does not change




Clock = 0: L1 opaque


L2 transparent

When **CLK falls** (1→0),

Q gets *X*, *X* cannot change

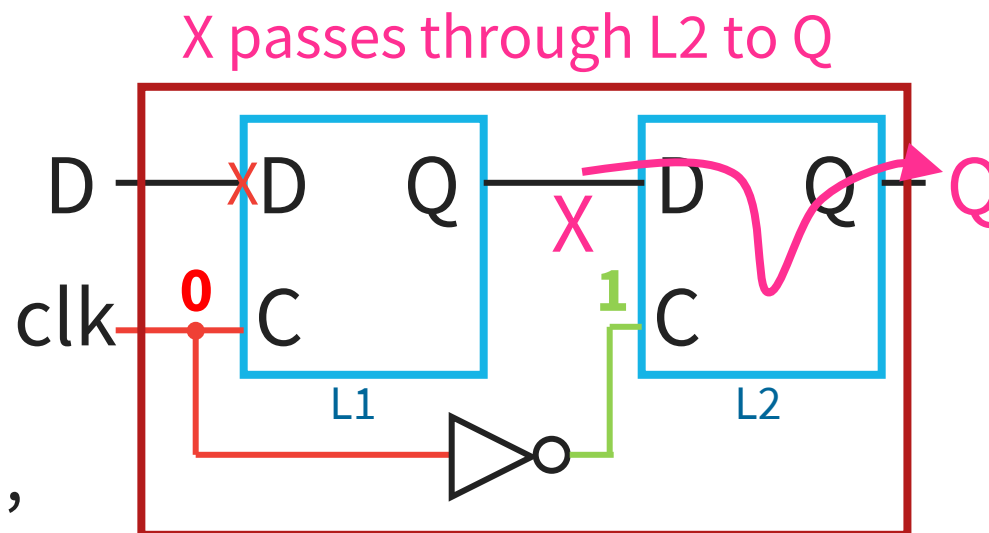


iClicker Question – start here

 


What is the value of Q at A & B?

 - a) $A = 0, B = 0$
- b) $A = 0, B = 1$
- c) $A = 1, B = 0$
- d) $A = 1, B = 1$




Building a D Flip Flop (DFF)

 


Step 1: Create an SR Latch

Set	Reset	Q
0	0	Q
0	1	0
1	0	1
1	1	?

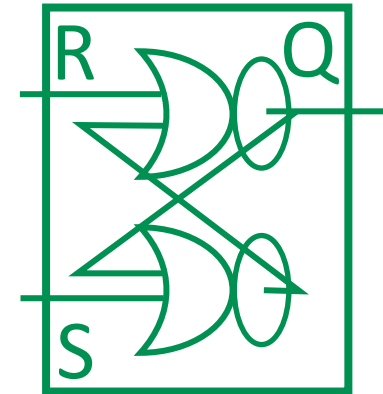


Building a D Flip Flop (DFF)

 


Step 1: Create an SR Latch

Step 2: Create a D Latch

Clk	Data	Q
0	0	Q
0	1	Q
1	0	0
1	1	1

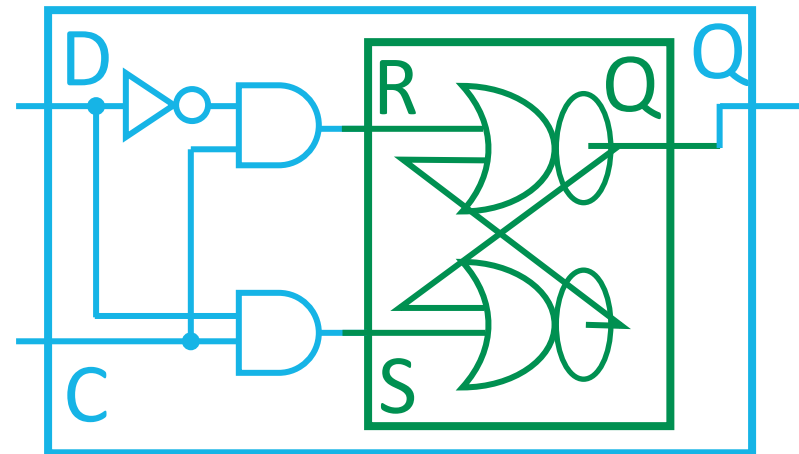


Building a D Flip Flop (DFF)

 

Step 1: Create an SR Latch

Step 2: Create a D Latch

 Step 3: Duplicate the D Latch, chain together



Takeaway



Set-Reset (SR) Latch can store one bit and we can change the value of the stored bit. But, SR Latch has a forbidden state.



(Unclocked) D Latch can store and change a bit like an SR Latch while avoiding a forbidden state.




An Edge-Triggered D Flip-Flop (aka Master-Slave D Flip-Flop) stores one bit. The bit can be changed in a synchronized fashion on the edge of a clock signal.

Next Goal

How do we store more than one bit, N bits?


Registers

 

Register


- D flip-flops in parallel

Registers

 


Register

 - D flip-flops in parallel
- shared clock
- extra clocked inputs: write_enable, reset, ...




Registers

 

Register

 - D flip-flops in parallel
- shared clock
- extra clocked inputs: write_enable, reset, ...



Takeaway


Set-Reset (SR) Latch can store one bit and we can change the value of the stored bit. But, SR Latch has a forbidden state.

(Unclocked) D Latch can store and change a bit like an SR Latch while avoiding a forbidden state.

An Edge-Triggered D Flip-Flop (aka Master-Slave D Flip-Flop) stores one bit. The bit can be changed in a synchronized fashion on the edge of a clock signal.


An N -bit register stores N -bits. It is created with N D-Flip-Flops in parallel along with a shared clock.

Registers

 


Register

 - D flip-flops in parallel
- shared clock
- extra clocked inputs: write_enable, reset, ...




Big Picture: How to Design a Processor

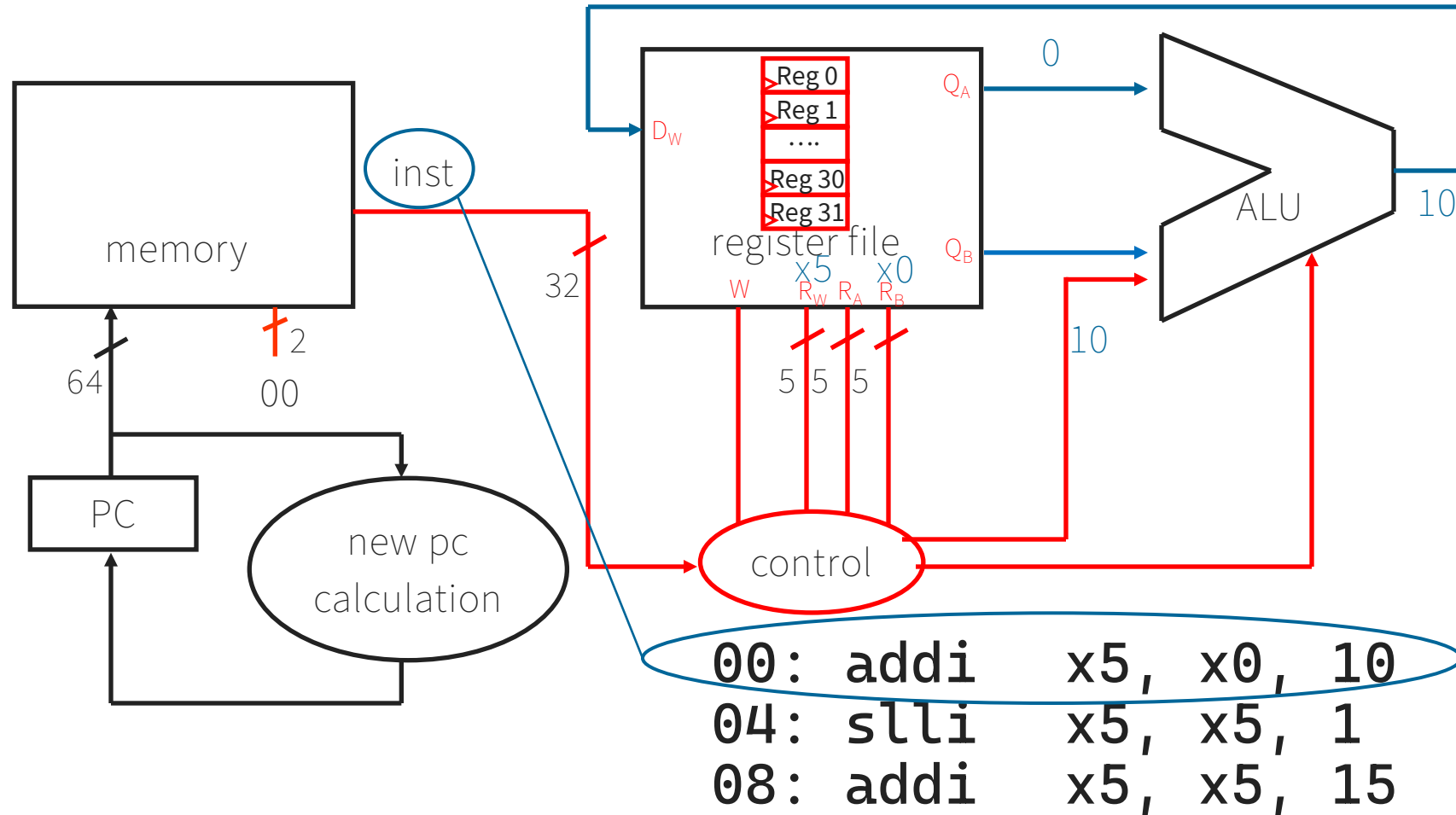

Big Picture: How to Design a Processor

Register File

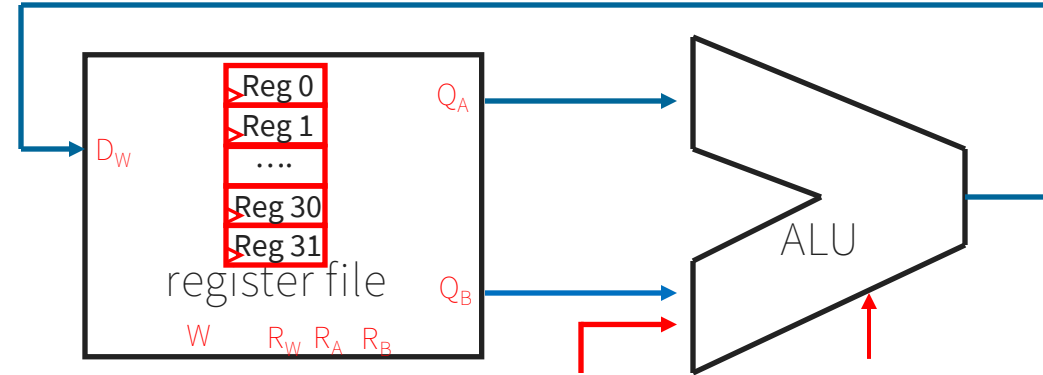- N read/write registers
- Indexed by register number




Registers

- Numbered from 0 to 31.
- Can be referred by number: x0, x1, x2, ... x31
 - May also see \$0, \$1, \$2 or r0, r1, r2
- Convention, each register also has a name:
 - x16 - x23 → s0-s7 ("s registers")
 - x8 - x15 → t0 - t7 ("t registers")

```
00: addi    x5, x0, 10
04: slli    x5, x5, 2
08: addi    x5, x5, 15
```



Big Picture: How to Design a Processor

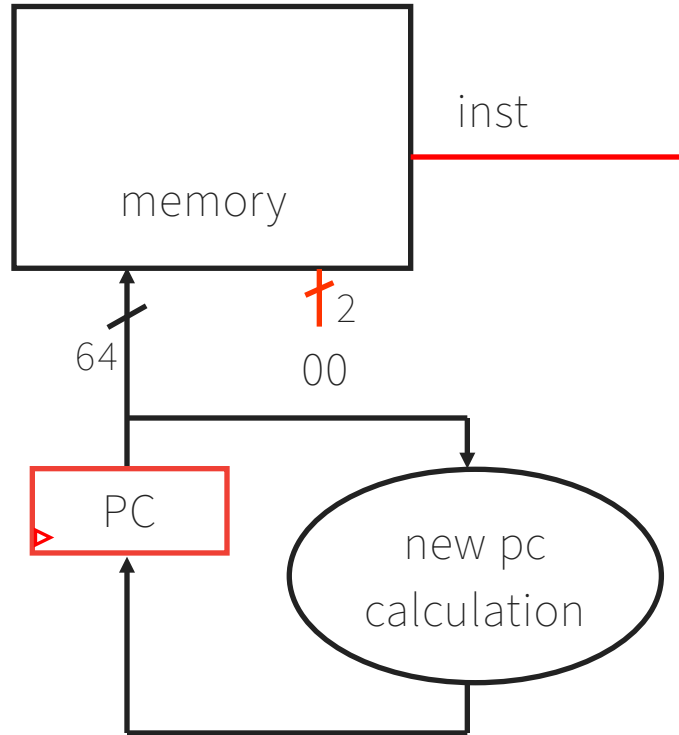


PC is register!

- PC is the Program Counter
- Stores the memory address of the next instruction

```
00: addi    x5, x0, 10
04: slli    x5, x5, 1
08: addi    x5, x5, 15
```



Big Picture: How to Design a Processor

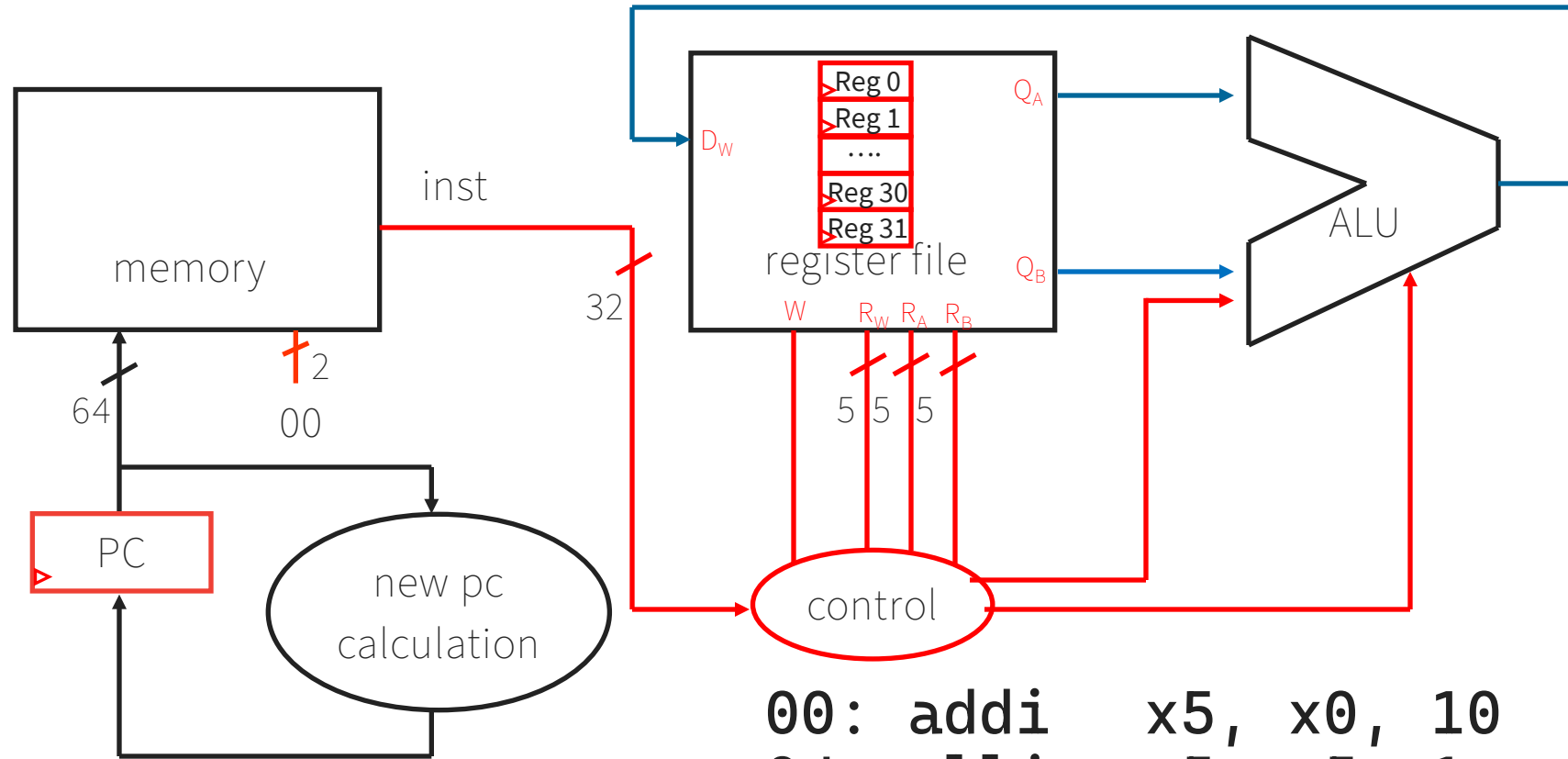

```

00: addi    x5, x0, 10
04: slli   x5, x5, 1
08: addi   x5, x5, 15
    
```



Takeaway

Set-Reset (SR) Latch can store one bit and we can change the value of the stored bit. But, SR Latch has a forbidden state.

(Unclocked) D Latch can store and change a bit like an SR Latch while avoiding a forbidden state.

An Edge-Triggered D Flip-Flop (aka Master-Slave D Flip-Flop) stores one bit. The bit can be changed in a synchronized fashion on the edge of a clock signal.

An N -bit register stores N -bits. It is created with N D-Flip-Flops in parallel along with a shared clock.

Summary

We store data values

- Stateful circuit elements (D Flip Flops, Registers, ...)
- Clock to synchronize state changes